

Reconfigurable architecture #2

osana@eee.u-ryukyu.ac.jp

This and next week


- * Basics of Verilog HDL
 - * Language to program logic circuit
 - * Simulator: to verify behavior in waveform
 - * Synthesis tool: generates equivalent circuit in gate-level

Module and port

- * In HDL, behavior is described per module basis
 - * Module has “ports” to connect outside
 - * A port is like a terminal
 - * From outside, we can't see inside a module
 - * A module can contain submodules (as blackbox)

Everything as modules

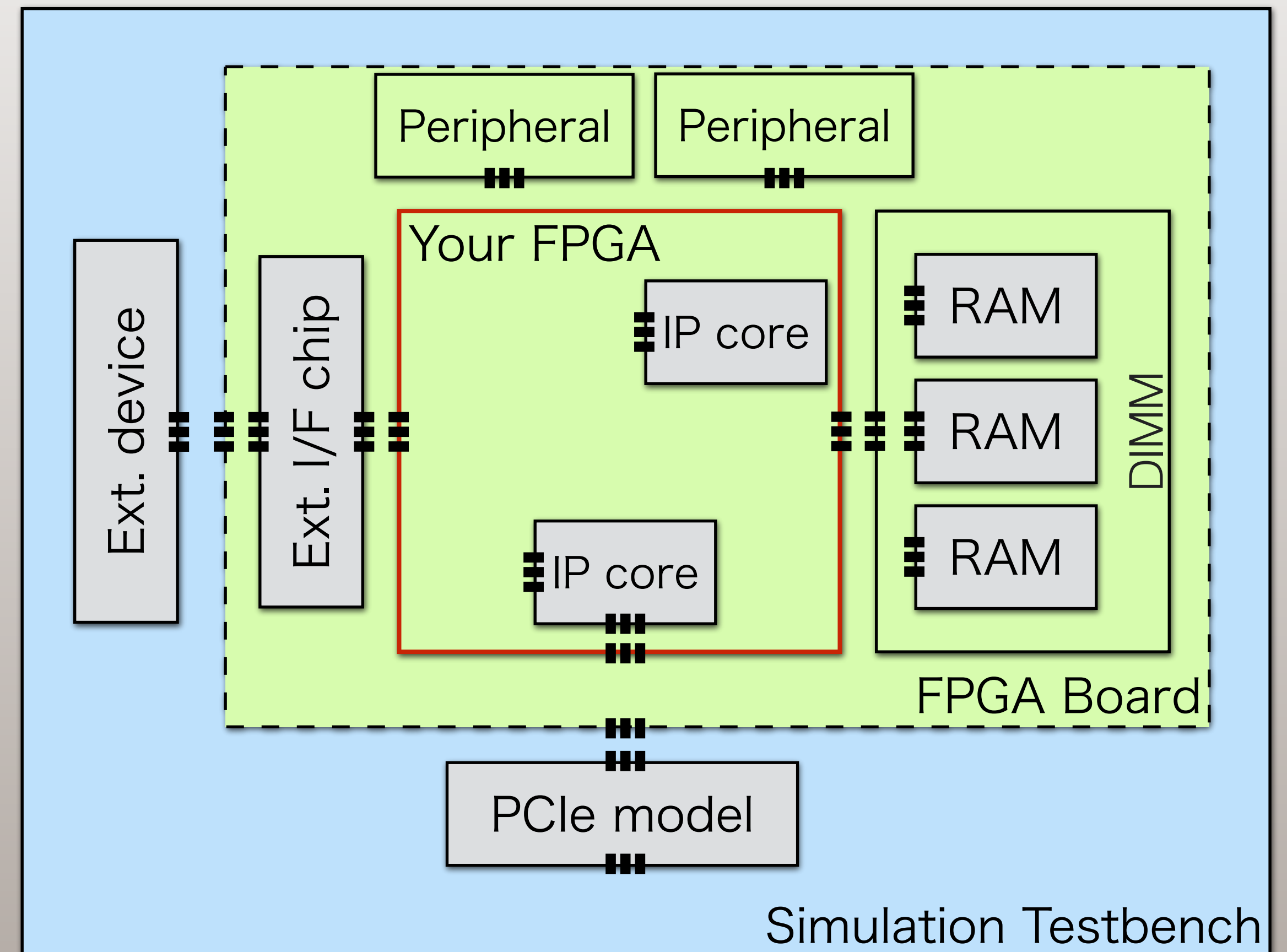- * FPGA design include
 - * Your HDL module + IP cores (imported design)
- * External device models in testbench



Tools and HDL syntax

- * Not all of HDL syntax is “synthesizable”
 - * Some syntax is valid only for simulation
 - * Used in testbench (we’ll see in later class)
- * At least, FPGA part must be written in “synthesizable” form

Writing HDL

- * Verilog HDL or VHDL
 - * “Logic circuit in gate level” is possible, but too hard
 - * “Writing RTL behavior” is easier and common
 - * RTL = Register Transfer Level
- * More recently, high-level synthesis (HLS) to generate RTLs from C/C++/Java is becoming popular

Gate level

- * Composed by “NAND”, “Flip-flop” or that kind of...
- * Must be optimized manually: Not realistic for large circuits
- * Or, obtained from RTL by “Logic synthesis”

RTL description

- * Do **what** if received this **signal** in this **state**
 - * Programmer can give any (meaningful) name to signals
 - * Some “software-like” syntax as “if” statement or conditional assignments
 - * No details about the final gate-level circuit is required

HDL as a programming language

- * HDL is uncommon as a programming language
 - * Programming language is usually about software
 - * Executed in “up-to-down” manner
- * HDL describes components, continue working all the time
 - * No beginning or end in HDL world!

Logic synthesis

- * Optimal design for each device technology
- * NAND gates are not almighty
- * Every LSI process and every FPGA have different logic cells
 - * Synthesis tools **maps** RTL to the logic cell libraries
 - * HDL is (basically) common to all device technologies

How to learn HDL


- * Syntax: basically same to logic circuit
 - * Combinational and sequential logic
- * HDL specific stuff:
 - * Module hierarchy and simulation
 - * ... and system organization is much more difficult

Schedule

- * Episode 1: Module, Combinational circuit and Operators
 - * + Design constraints
- * Episode 2: Sequential logic and Hierarchical design
- * Episode 3: Simple testbench and Running simulation

Goal of the day

 - * LEDs and slide SWs
- * With logic gates intermediate
- * 16 LEDs and SWs on board
- * Also try using push SW
- * First of all, let's see the syntax



Literals

- * 123: “Normal” numbers are interpreted as a (32bits) decimal
- * 32'h1234abcd : Hexadecimal “1234abcd” of 32bits
 - * b: binary, d: decimal, h: hexadecimal
 - * Inserting “_” between any columns is allowed for better readability
 - * example: 32'h1234_abcd
- * Single bit of “1” means “True”, “0” is “False”
 - * Vector signal is “False” if all bits are 0

Module and port

- * Module definition

- * starts by “module”


- * ends by “endmodule”

- * endmodule has no “.”

```
module module_name ( ports );  
    . . .  
endmodule
```


Module and port

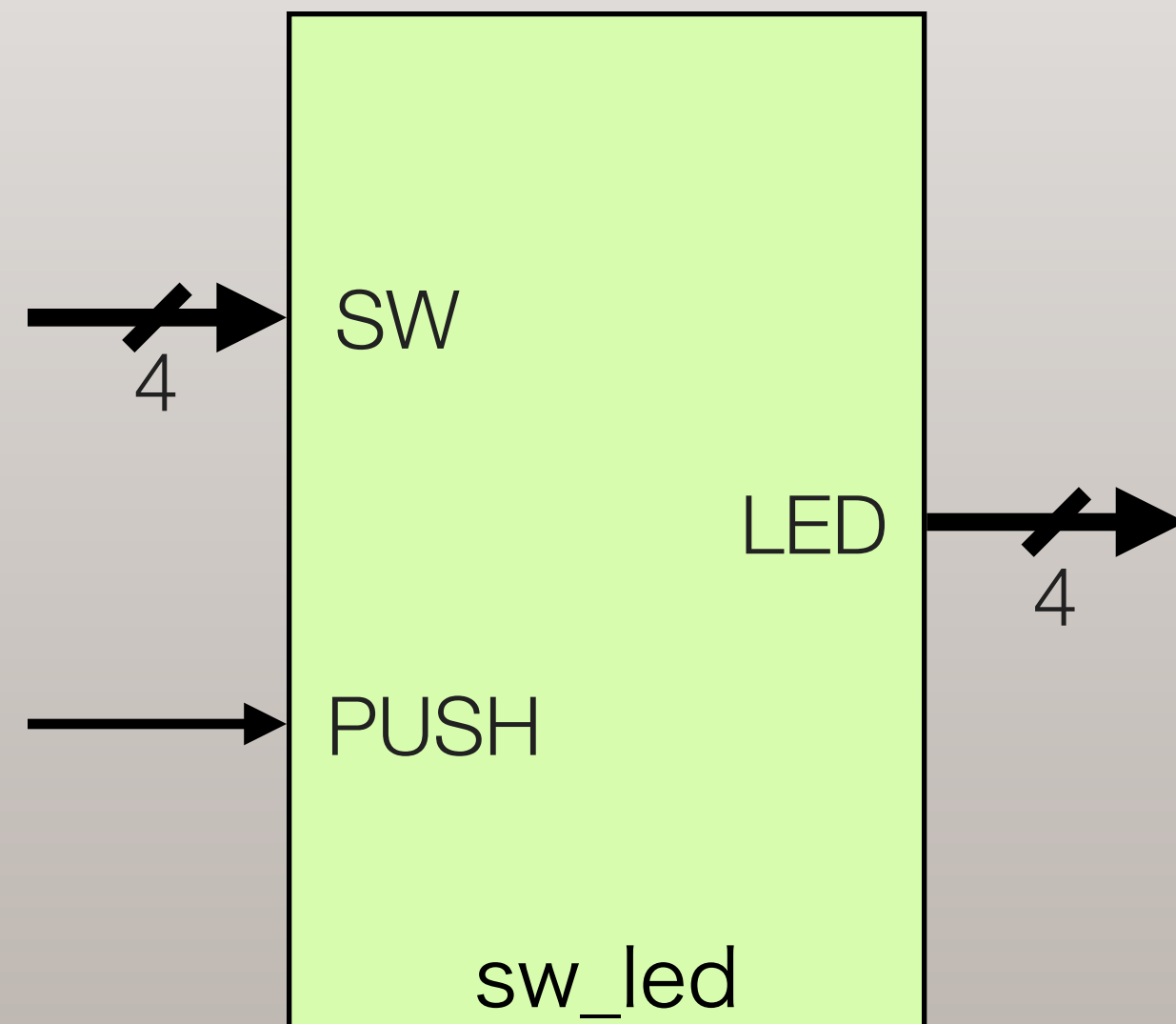Signal has 4 bits,
LSB is numbered as “0”



```
module sw_led
(
    input  wire [3:0] SW,
    input  wire      PUSH,
    output wire [3:0] LED
);
    . . .
endmodule
```


Continuous assignment

- * Assignments in software:
 - * Happens when executed
- * In hardware:
 - * Happens continuously (because it's wired)

```
module sw_led
(
    input  wire [3:0] SW,
    input  wire      PUSH,
    output wire [3:0] LED
);


    assign LED = SW;

endmodule
```

 

Ex1: Basic logic gates

* AND, NOT, OR gates

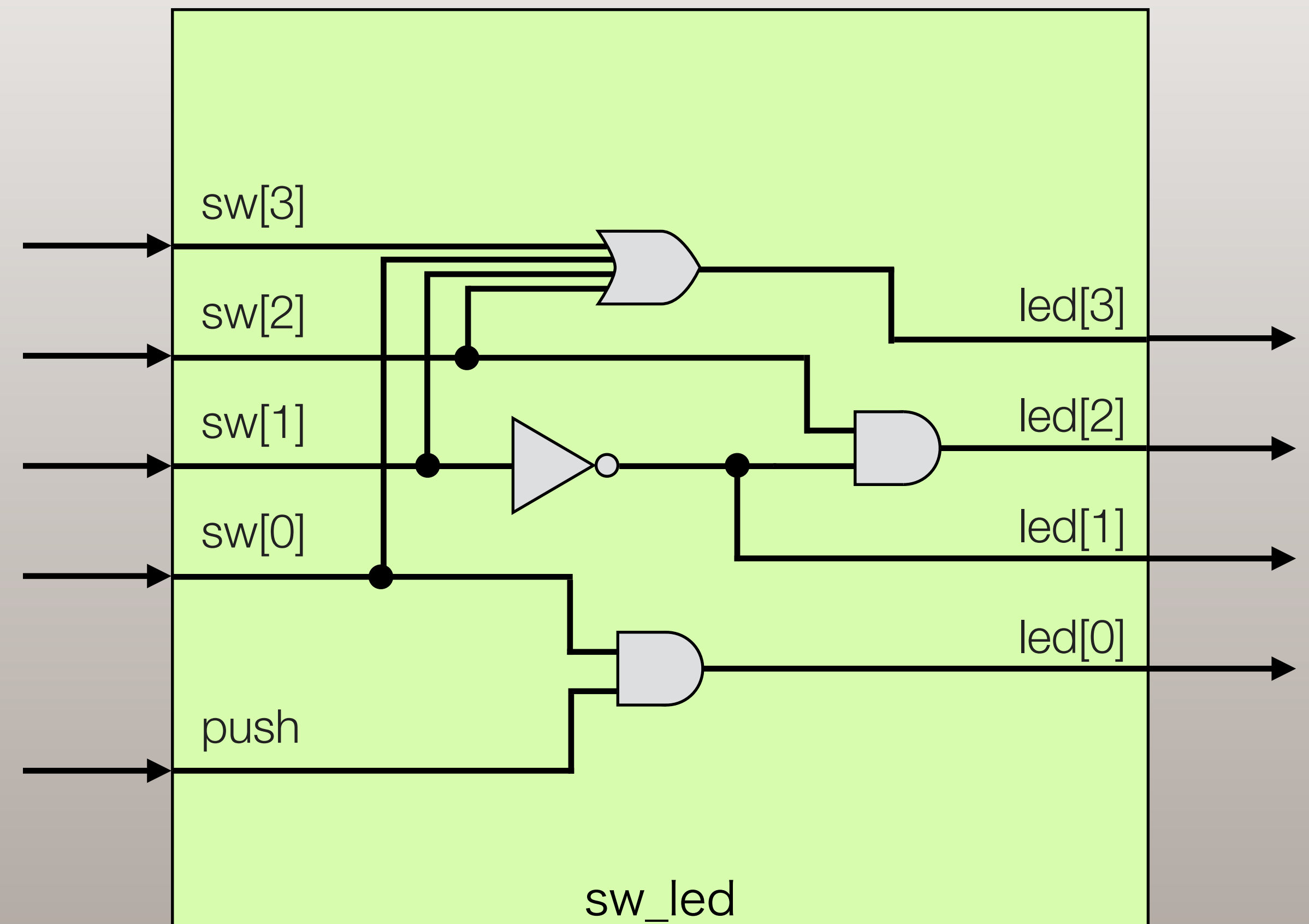


Logic operators

* AND: "&", OR: "|", NOT "~"

```
module sw_led
(
    input wire [3:0] SW,
    input wire      PUSH,
    output wire [3:0] LED
);

    assign LED[0] = PUSH & SW[0];
    assign LED[1] = ~SW[1];
    assign LED[2] = LED[1] & SW[2];

endmodule
```

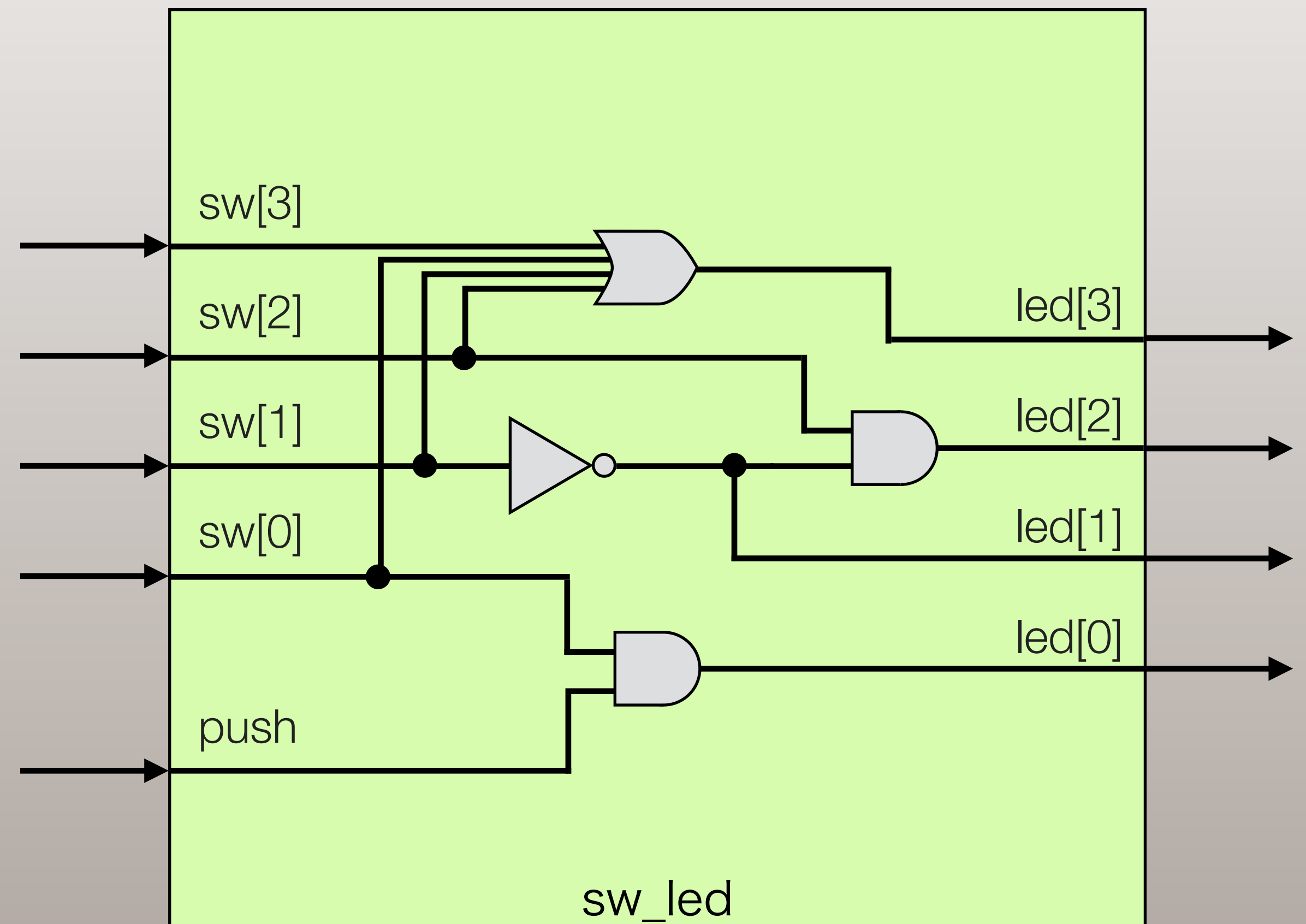


Name internal signals

- * “wire” type for assign statement

```
module sw_led
(
    input  wire [3:0] SW,
    input  wire      PUSH,
    output wire [3:0] LED
);

    wire  SW1_;
    assign SW1_ = ~SW[1];
    assign LED[1] = SW1_;
    assign LED[2] = SW1_ & SW[2];

endmodule
```

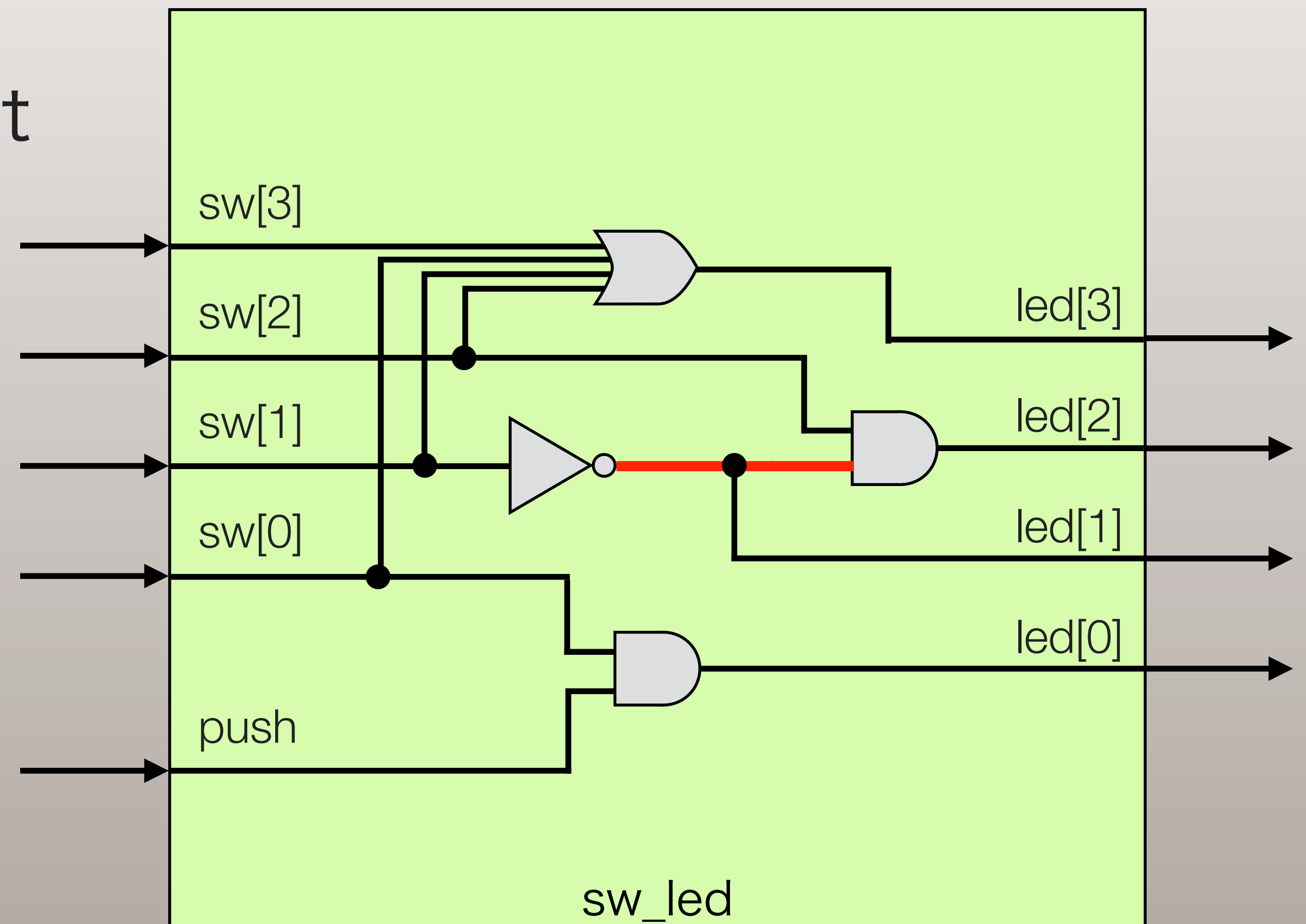

Name internal signals

- * Assignment can be done within wire declaration

```
module sw_led
(
    input  wire [3:0] SW,
    input  wire      PUSH,
    output wire [3:0] LED
);

wire    SW1_;
assign SW1_ = ~SW[1];
assign LED[1] = SW1_;
assign LED[2] = SW1_ & SW[2];

endmodule
```

```
module sw_led
(
    input  wire [3:0] SW,
    input  wire      PUSH,
    output wire [3:0] LED
);

wire    SW1_ = ~SW[1];
assign LED[1] = SW1_;
assign LED[2] = SW1_ & SW[2];

endmodule
```


Reduction operator

- * LED[3]: Simplify or'ing call
- * Operator before signal

```
module sw_led
(
  input  wire [3:0] SW,
  input  wire      PUSH,
  output wire [3:0] LED
);


  assign LED[3] = |SW;

endmodule
```

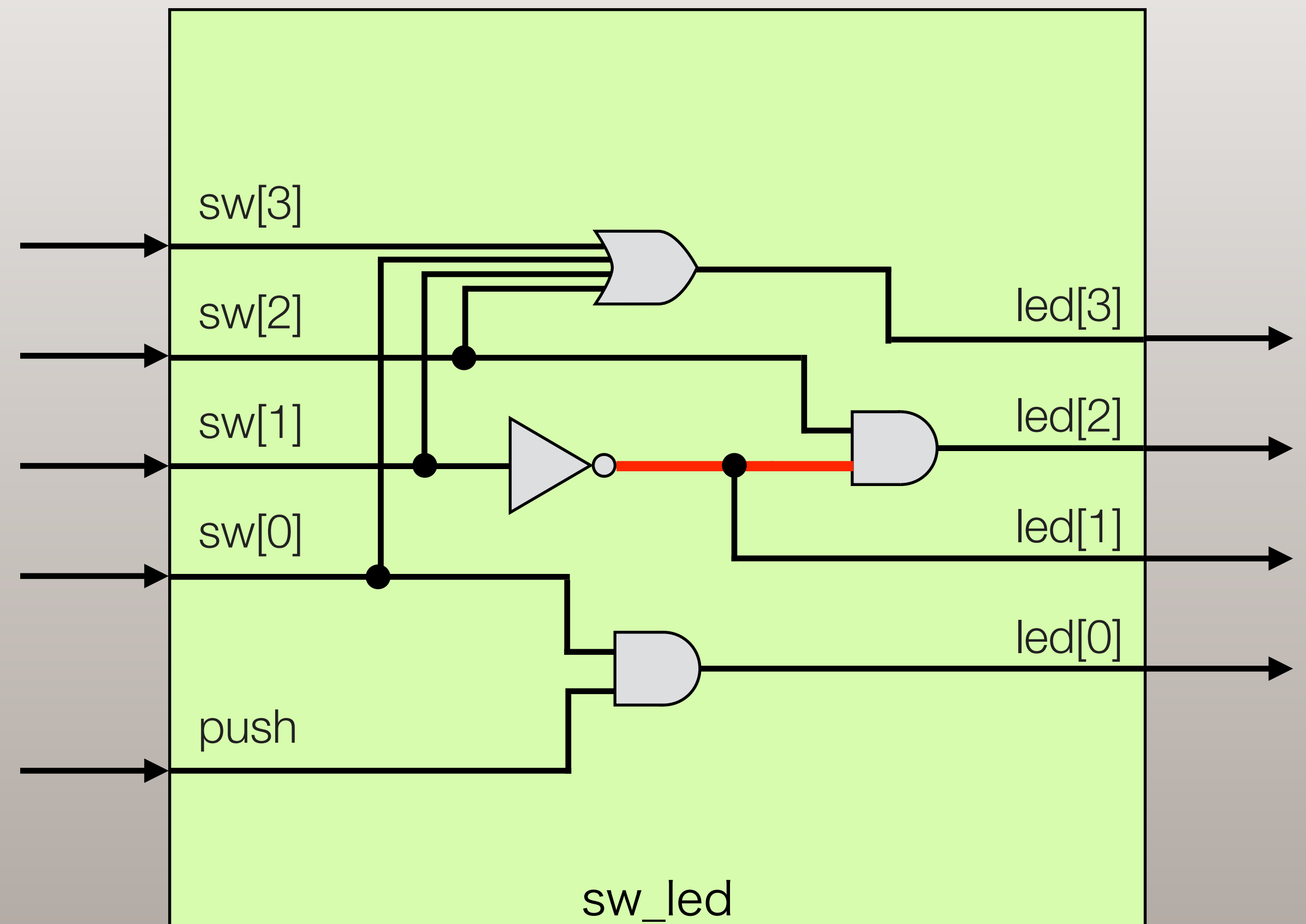

Ex 2: Multiplexer

- * 2-input MUX
 - * Not simple with logic operators
- * Conditional assignment
 - * `assign X = (cond) ? value : default_val;`
 - * Don't forget default value

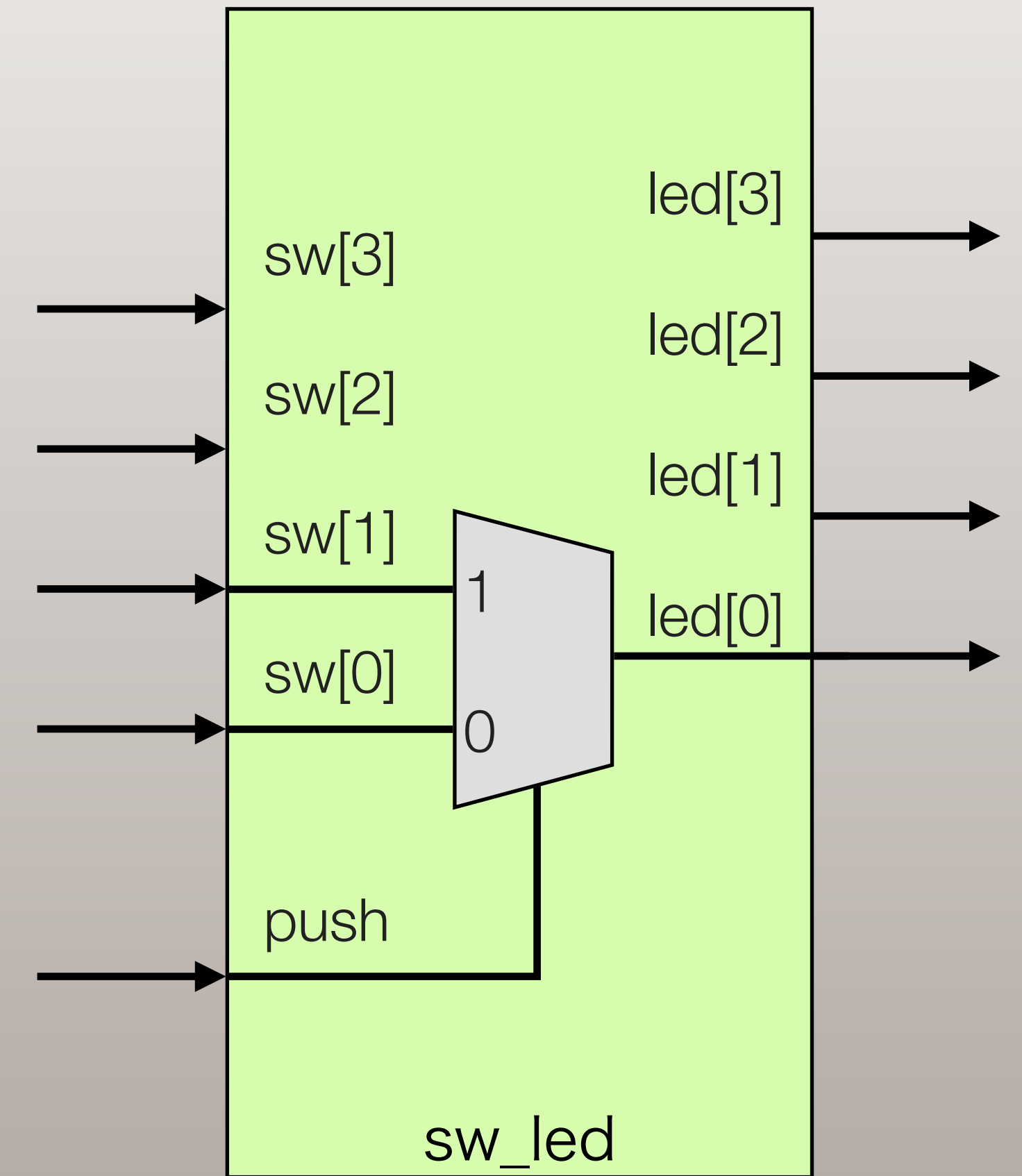


Ex 2: Multiplexer

- * Conditional assignment
- * `assign X = (cond) ? val : default_val;`

```
module sw_led
(
    input  wire [3:0] SW,
    input  wire      PUSH,
    output wire [3:0] LED
);


    assign LED[0] = PUSH ? SW[1] : SW[0];

endmodule
```

 

Ex2.5: Multi-input MUX

- * 2bit select signal

 

Signal decomposition and concatenation

- * [] to extract bit(s)
- * {} to concatenate
- * New “bundled” signal
- * Duplication:
{4{X}} is { X, X, X, X }

```
module sw_led
(
    input  wire [3:0] SW,
    input  wire      PUSH,
    output wire [3:0] LED
);

    wire [1:0] SEL;
    assign SEL = { SW[0], PUSH };

endmodule
```


Ex2.5: Multi-input MUX

- * Possible with conditional assignment

```
module sw_led
(
    input  wire [3:0] SW,
    input  wire      PUSH,
    output wire [3:0] LED
);

    wire [1:0] SEL;
    assign SEL = { SW[0], PUSH };
    assign LED[0] = (SEL==2'b00) ? SW[1] :
                   (SEL==2'b01) ? SW[2] :
                   SW[3];

endmodule
```

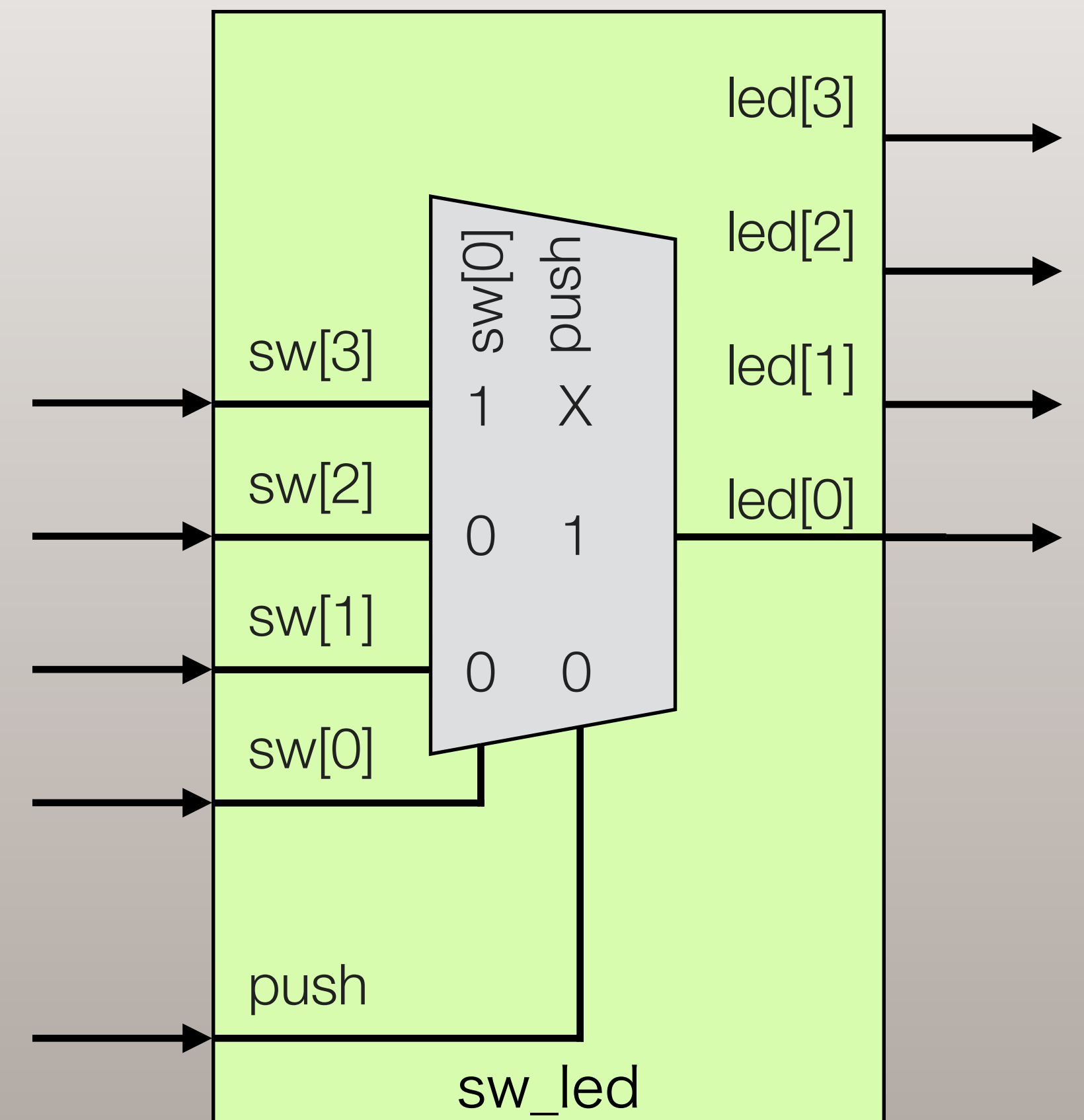

Conditional operations

- * Think about circuit!

- * Don't care is "x"

```
// Using don't care makes circuit smaller
assign X = ( A == 3'b1xx ) ? 3 :
           ( A == 3'b01x ) ? 2 :
           ( A == 3'b001 ) ? 1 : 0;
```

- * For correctness:

```
// Adder is synthesized: slow and large
assign X = ( A < 100 ) ? B : C;
```

- * Write default value



```
// With priority: slow
assign X = COND1 ? ( COND2 ? A : B ) : C;
```

- * Check consistency of conditions


```
// Not mutually exclusive: will be broken
assign X = ( A[3:2] == 2'b10 ) ? 1 :
           ( A[1:0] == 2'b11 ) ? 2 : 3;
```


Gates and Delays

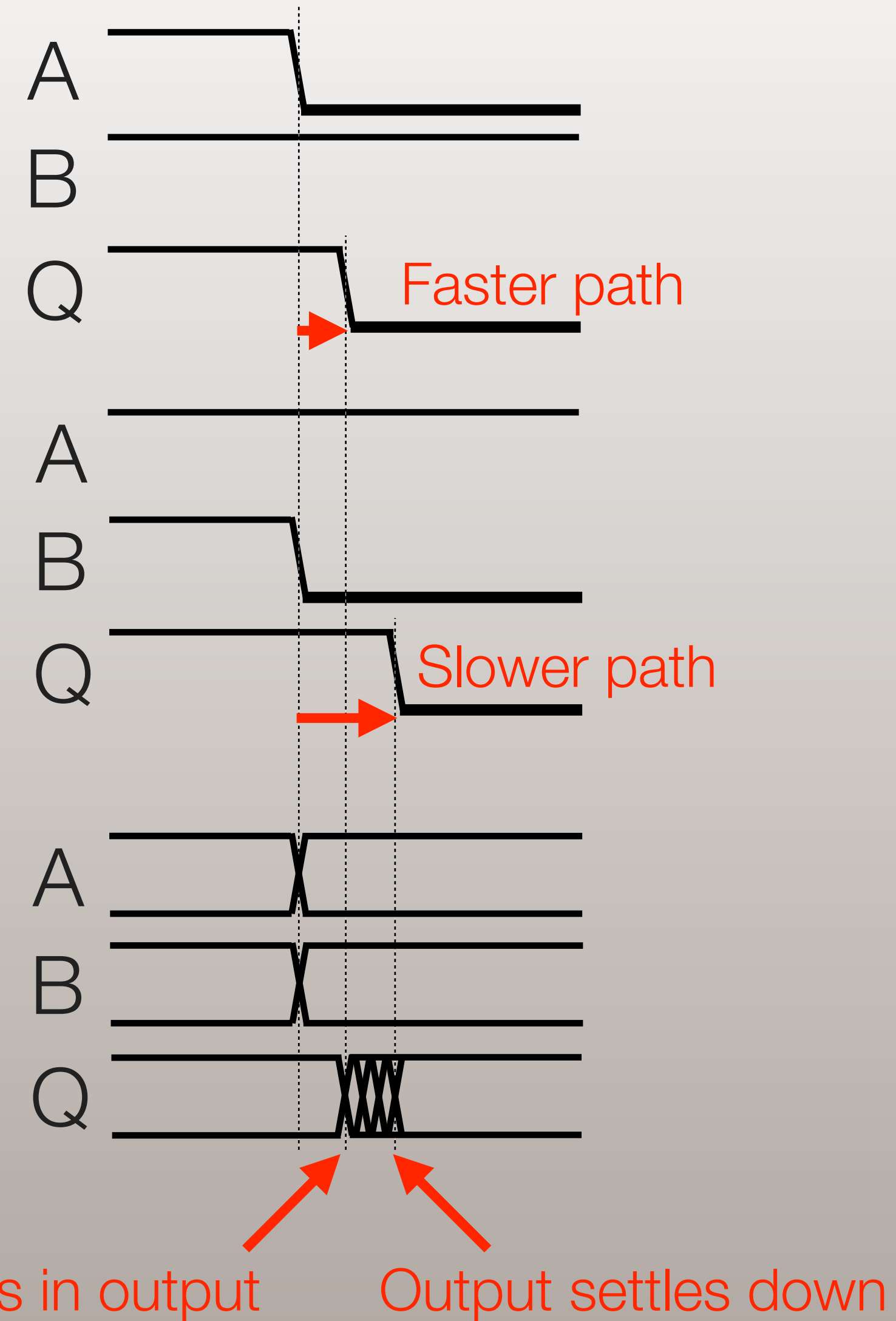 - * Input / Output transitions
- * Gate and wire delay
- * Different input causes different delay time
- * Contamination delay and Propagation delay



Think about resulting circuit

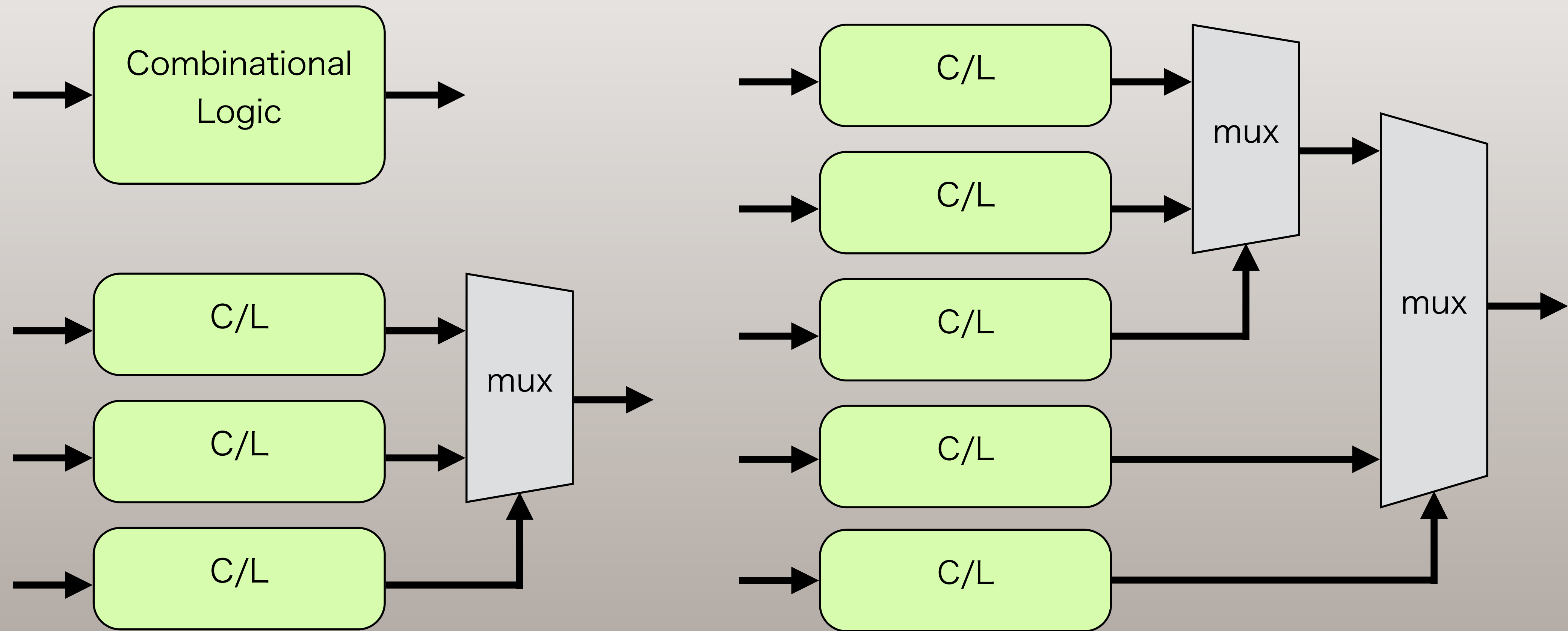

Condition affects on # inputs of MUX and # MUX stages

All above is about “Internals”


- * Thinking about “inside” of the FPGA is not sufficient
- * Let's see signal pins of the FPGAs

FPGA is general-purpose


- * Some flexibility of using signal pins
 - * “Dedicated” pins such as power supplies and startup
 - * “User I/O” pins that are fully programmable
 - * “Multi-purpose” pins for user I/O but some special capability such as clock inputs

Front and back of the chip

 CS/CSG324 and CS/CSG325 Wire-Bond Chip-Scale BGA Artix-7 FPGAs (0.8 mm Pitch)




Xilinx UG475より

 

BGA (Ball Grid Array) is popular: pins are regularly arranged solder balls

Pin maps

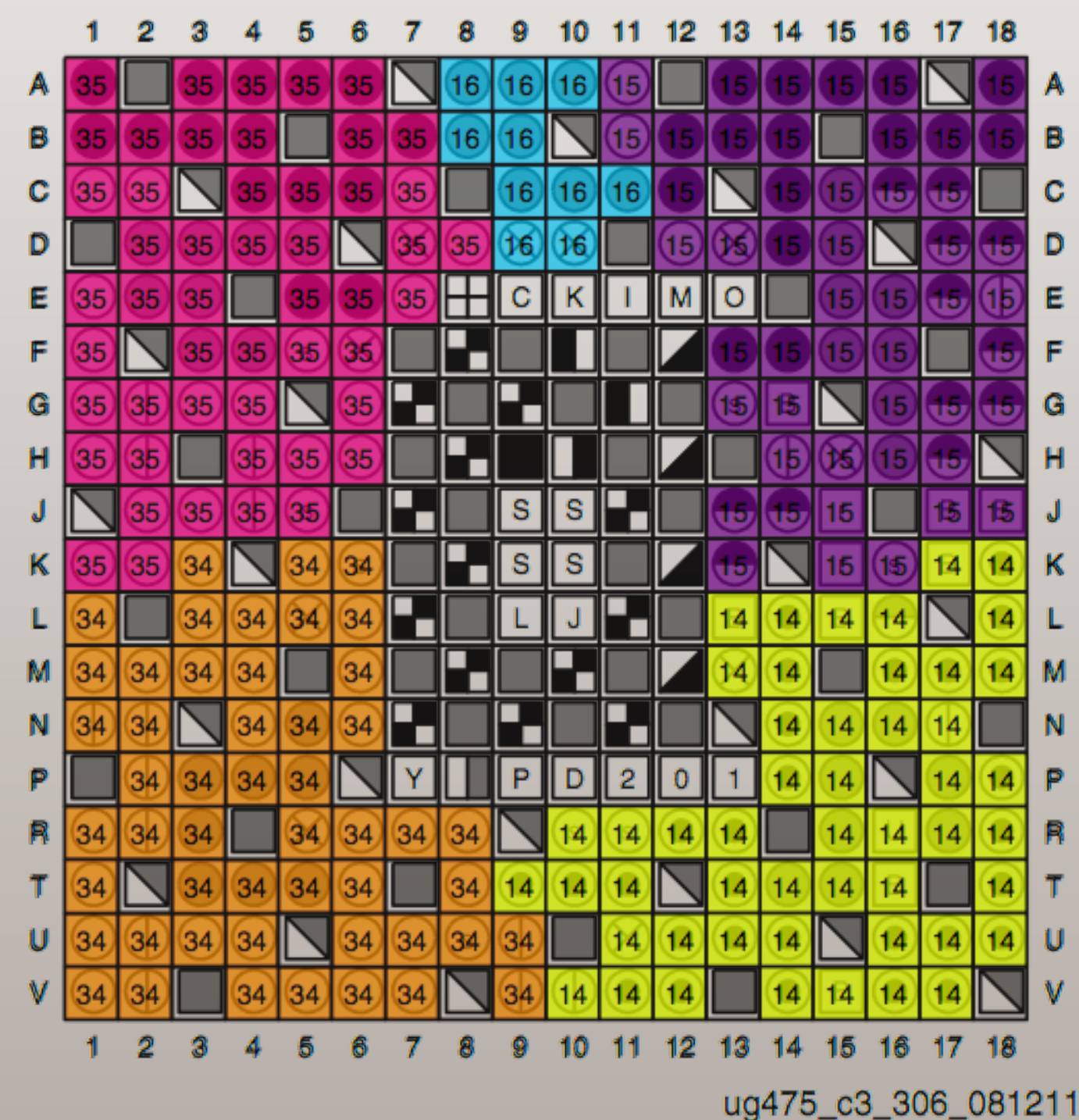

User I/O Pins	Dedicated Pins	Other Pins
<div><div>○</div>IO_LXXY_#</div> <div><div>○s</div>IO_XX_#</div>	<div><div>C</div>CCLK_0</div> <div><div>S</div>VP_0</div> <div><div>D</div>DONE_0</div> <div><div>S</div>VN_0</div> <div><div>J</div>DXP_0</div> <div><div>S</div>VREFP_0</div> <div><div>L</div>DXN_0</div> <div><div>S</div>VREFN_0</div> <div><div>Y</div>INIT_B_0</div> <div><div>0</div>M0_0</div> <div><div>1</div>M1_0</div> <div><div>2</div>M2_0</div> <div><div>P</div>PROGRAM_B_0</div> <div><div>K</div>TCK_0</div> <div><div>I</div>TDI_0</div> <div><div>O</div>TDO_0</div> <div><div>M</div>TMS_0</div> <div><div>VCCADC_0</div></div> <div><div>VCCBATT_0</div></div>	<div><div>GND</div></div> <div><div>VCCAUX_IO_G#</div></div> <div><div>VCCAUX</div></div> <div><div>VCCINT</div></div> <div><div>VCCO_#</div></div> <div><div>VCCBRAM</div></div> <div><div>NC</div></div>
Multi-Function Pins		
<div><div>B</div>ADV_B</div> <div><div>B</div>FCS_B</div> <div><div>B</div>FOE_B</div> <div><div>B</div>MOSI</div> <div><div>B</div>FWE_B</div> <div><div>B</div>DOUT_CSO_B</div> <div><div>B</div>CSI_B</div> <div><div>B</div>PUDC_B</div> <div><div>U</div>RDWR_B</div> <div><div>r</div>RS0-RS1</div> <div><div>AD0P/AD0N-AD15P/AD15N</div></div> <div><div>EMCCLK</div></div>	<div><div>⊕</div>VRN</div> <div><div>⊖</div>VRP</div> <div><div>⊗</div>VREF</div> <div><div>●</div>D00-D31</div> <div><div>●</div>A00-A28</div> <div><div>⊖</div>DQS</div> <div><div>●</div>MRCC</div> <div><div>●</div>SRCC</div>	



ug475_c3_305_090711

Colored are user I/O pins, different colors are I/O banks

Pin arrangement and designer

- * Required to read the data sheet carefully if:
 - * You're designing FPGA board
 - * Connecting something to board's GPIO (General Purpose I/O)
- * Otherwise, we have to just know “what is connected to which pin”
 - * Using off-the-shelf board is (mostly) this

Pin assignment: Schematics

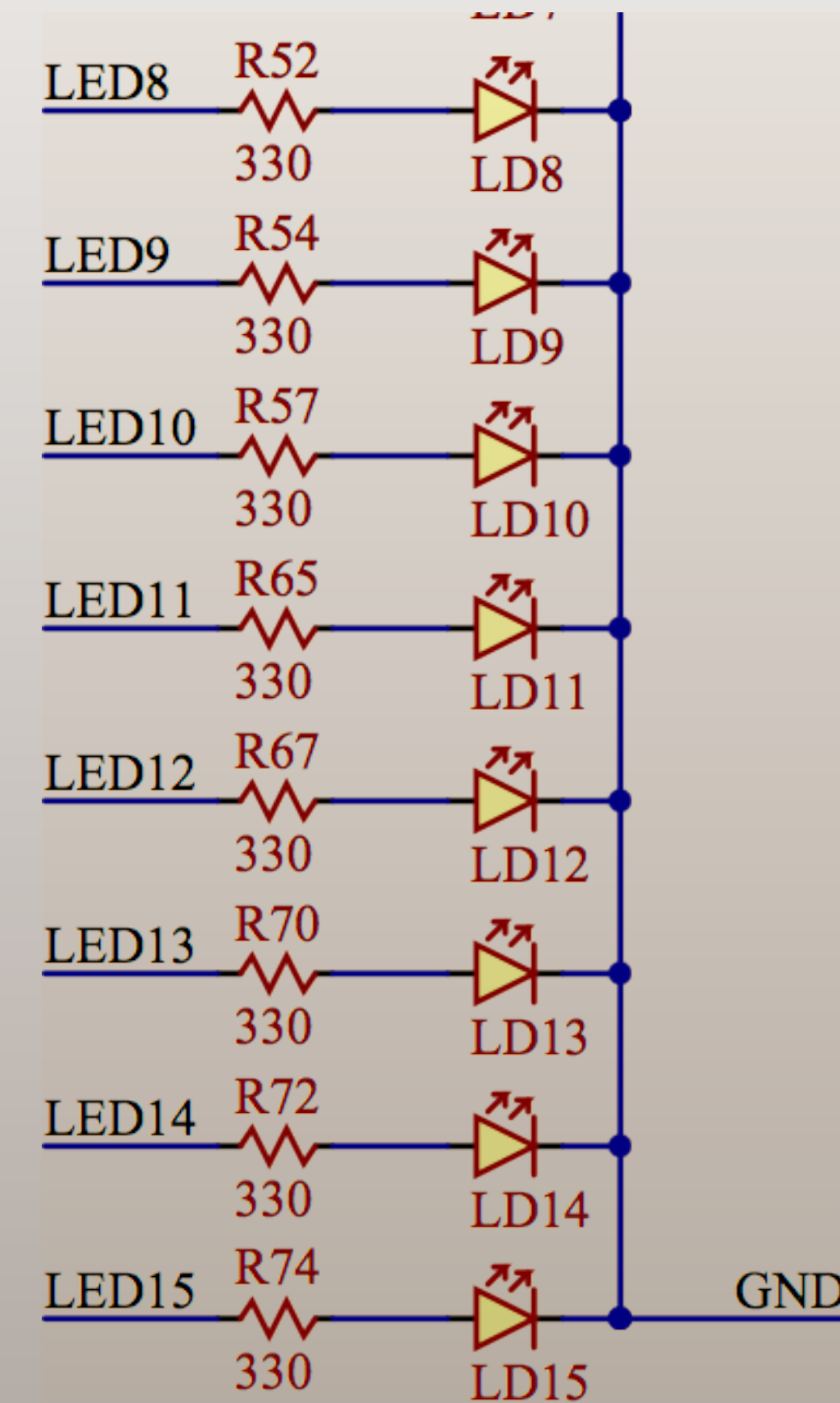 


Pin assignemnt: Schematics

IC8D

BANK 34		
LED17 R K6	IO_0_34	IO_L1P_T0_34
SW1 U8	IO_25_34	IO_L1N_T0_34
		IO_L2P_T0_34
		IO_L2N_T0_34
		IO_L3P_T0_DQS_34
		IO_L3N_T0_DQS_34
		IO_L4P_T0_34
		IO_L4N_T0_34
		IO_L5P_T0_34
		IO_L5N_T0_34
		IO_L6P_T0_34
		IO_L6N_T0_VREF_34
		IO_L7P_T1_34
		IO_L7N_T1_34
		IO_L8P_T1_34
		IO_L8N_T1_34
		IO_L9P_T1_DQS_34
		IO_L9N_T1_DQS_34
		IO_L10P_T1_34
		IO_L10N_T1_34
		IO_L11P_T1_SRCC_34
		IO_L11N_T1_SRCC_34
		IO_L12P_T1_MRCC_34
		IO_L12N_T1_MRCC_34
		IO_L13P_T2_MRCC_34
		IO_L13N_T2_MRCC_34
		IO_L14P_T2_SRCC_34
		IO_L14N_T2_SRCC_34
		IO_L15P_T2_DQS_34
		IO_L15N_T2_DQS_34
		IO_L16P_T2_34
		IO_L16N_T2_34
		IO_L17P_T2_34
		IO_L17N_T2_34
		IO_L18P_T2_34
		IO_L18N_T2_34
		IO_L19P_T3_34
		IO_L19N_T3_VREF_34
		IO_L20P_T3_34
		IO_L20N_T3_34
		IO_L21P_T3_DQS_34
		IO_L21N_T3_DQS_34
		IO_L22P_T3_34
		IO_L22N_T3_34
		IO_L23P_T3_34
		IO_L23N_T3_34
		IO_L24P_T3_34
		IO_L24N_T3_34

XC7A100T-xCSG324C

 

Constraints

- * Pin assignments are not described by HDL
 - * Given to CAD tools as “implementation constraints”
 - * Independent file from HDL
- * Pin number, voltage, clock frequency, etc.

XDC constraints (Vivado)

```
module sw_led
(
    input [3:0] SW,
    input      PUSH );

set_property PACKAGE_PIN U9 [get_ports SW [0]]
set_property PACKAGE_PIN U8 [get_ports SW [1]]
set_property PACKAGE_PIN R7 [get_ports SW [2]]
set_property PACKAGE_PIN R6 [get_ports SW [3]]
set_property IOSTANDARD LVCMOS33 [get_ports {SW[*]}]

set_property PACKAGE_PIN E16 [get_ports PUSH]
set_property IOSTANDARD LVCMOS33 [get_ports PUSH]
```

UCF constraints (ISE: obsolete)

```
module sw_led
(
    input [3:0] SW,
    input      PUSH );

NET "SW[0]" LOC = U9;
NET "SW[1]" LOC = U8;
NET "SW[2]" LOC = R7;
NET "SW[3]" LOC = R6;
NET "SW[*]" IOSTANDARD = LVCMOS33;

NET "PUSH" LOC = E16 | IOSTANDARD = LVCMOS33;
```