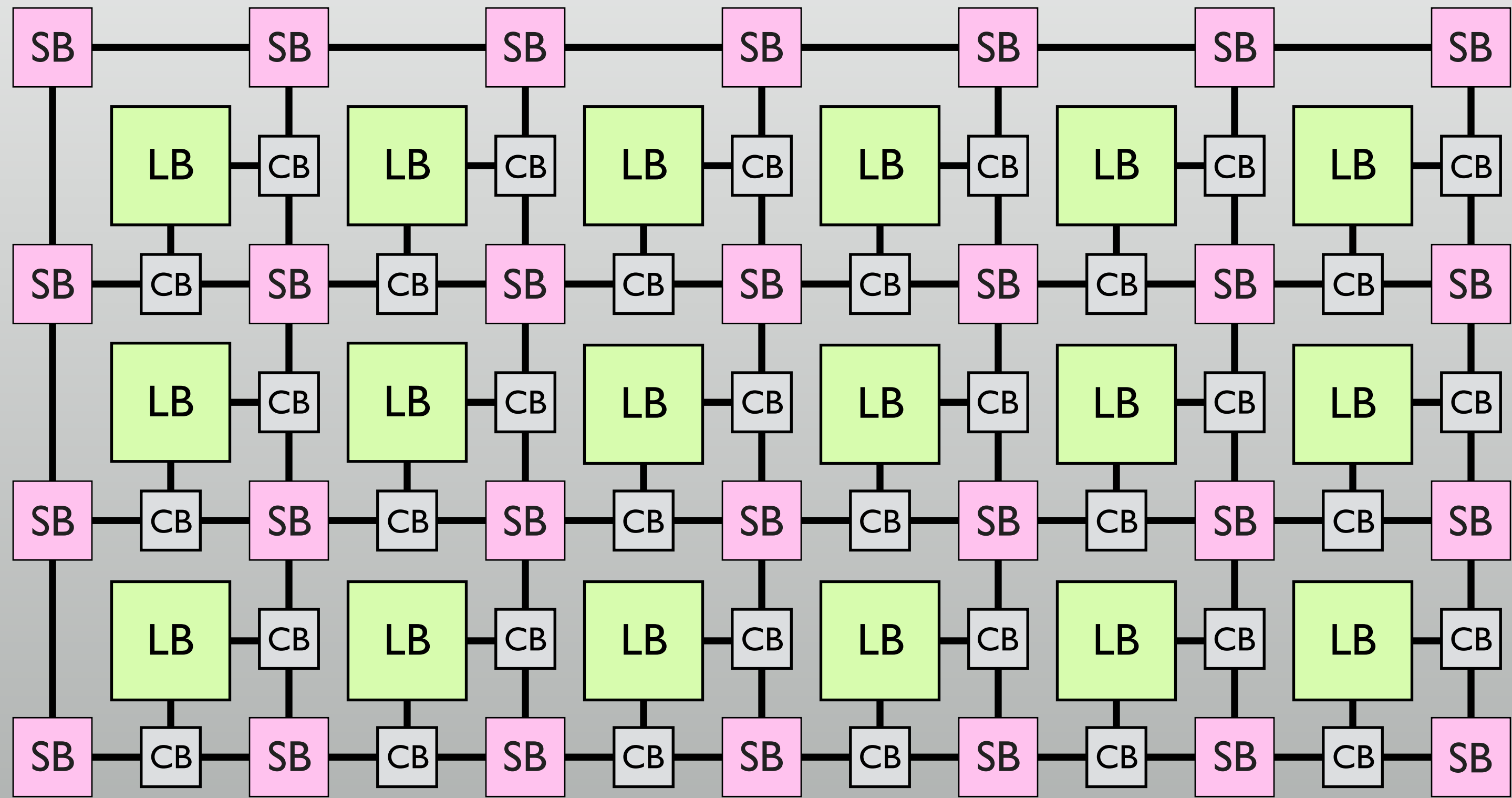


# **Reconfigurable Architecture (12)**

FPGA Architecture


# Basic components

- \* LB: Logic Block
- \* CB: Connection Block
- \* SB: Switch Block
- \* Interconnect wires



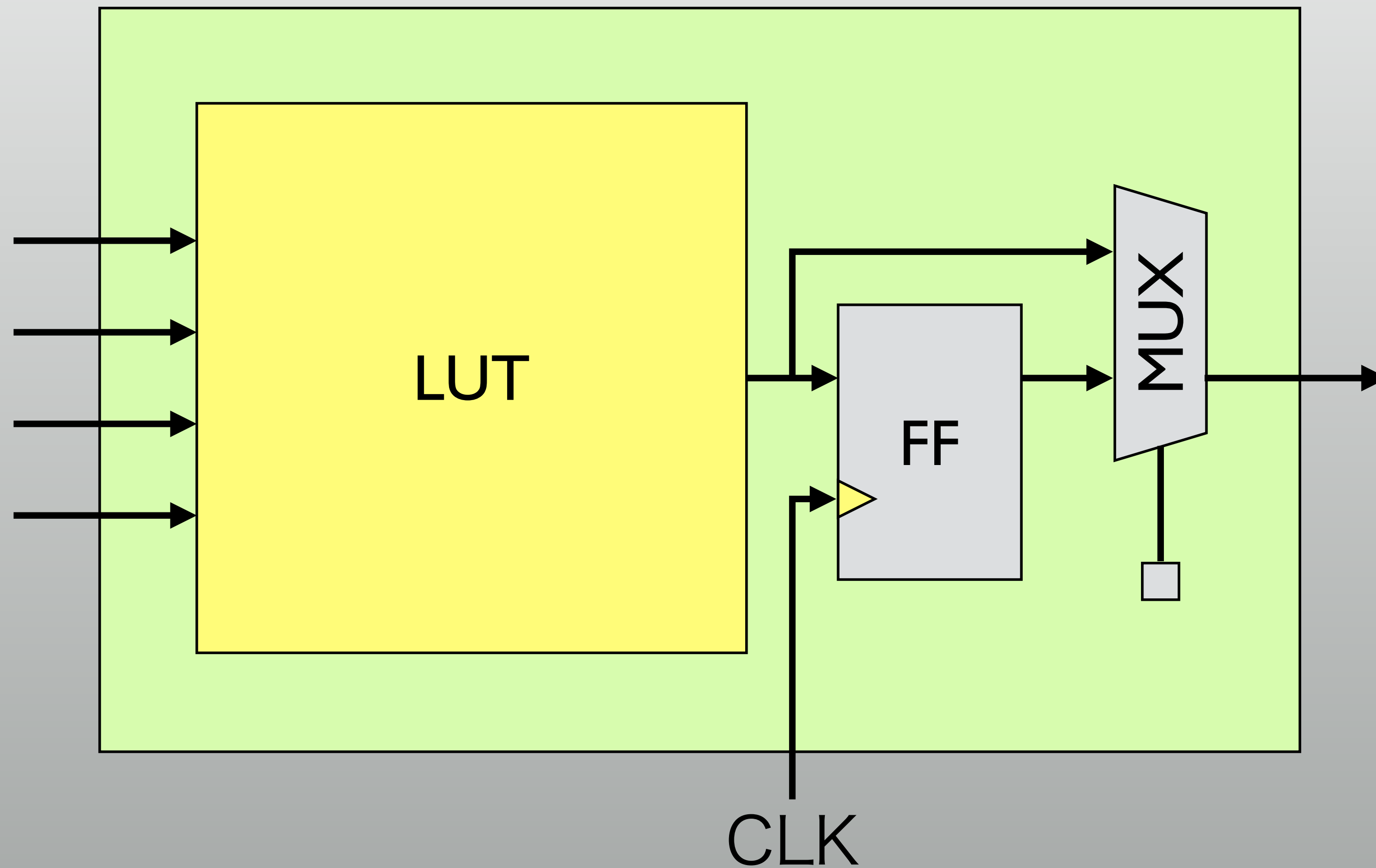
# Logic Block

- \* The very basic structure: LUT + FF + MUX



 
# Interconnect and SB

- \* Multiple horizontal & vertical wires
- \* Not fully-connected: destination wires are always limited to reduce # of switches in SB


 
# LB, CB and wires

- \* Connect wires from logic block pins to interconnect tracks
- \* Is not fully connected, because of the same reason




# Other components


- \* IOB (I/O Blocks)
- \* Clock buffers and interconnects
 
# I/O pads

- \* Wire bonding
  - \* I/O pads **around** the chip
  - \* Long wires to the pads
- \* Flip-chip
  - \* Distributed I/O pads
  - \* Shorter logic wires and better power delivery



従来型

 


フリップチップ



 
# Clock tree

- \* Wires of exactly same length, from the clock inputs to all FFs on the FPGA
- \* Dedicated wires for clock, not the wires for logic



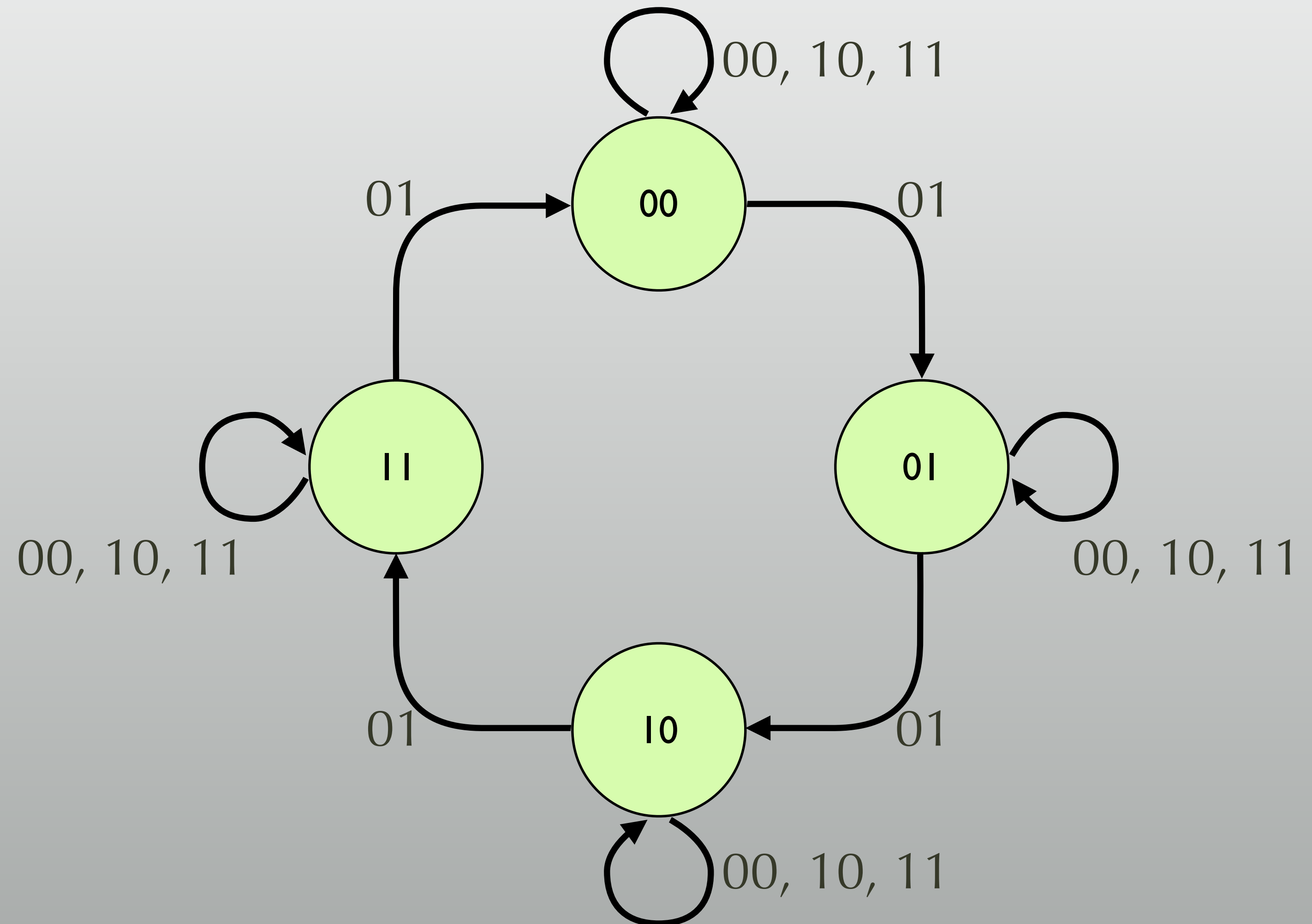
# Logic circuit in textbooks

- \* Combinational logic and FFs
- \* State transition diagrams



# Logic circuits in action

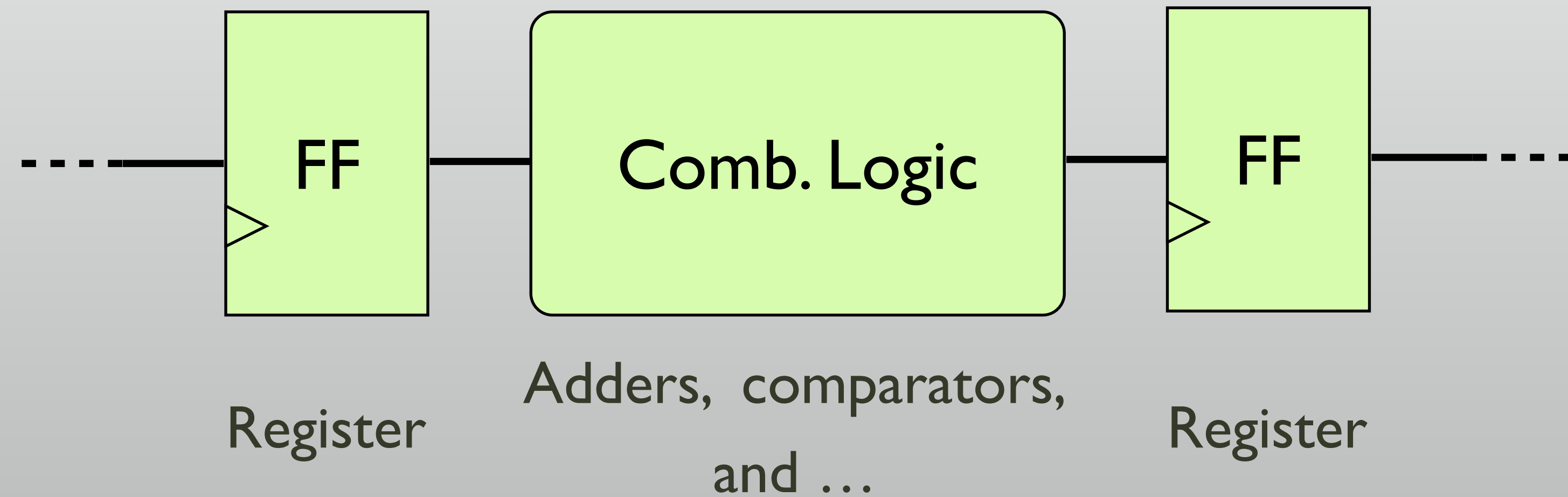

# Performance depends on:


- \* Number of register (FF) stages
  - \* = # of clock cycles to get the result
- \* Combinational delay = logic delay + wire delay
  - \* Clock frequency depends on the worst combinational delay

# Make common cases faster

- \* Effective way for basic building blocks, such as:
  - \* Adders
  - \* Shift registers
  - \* Memory elements

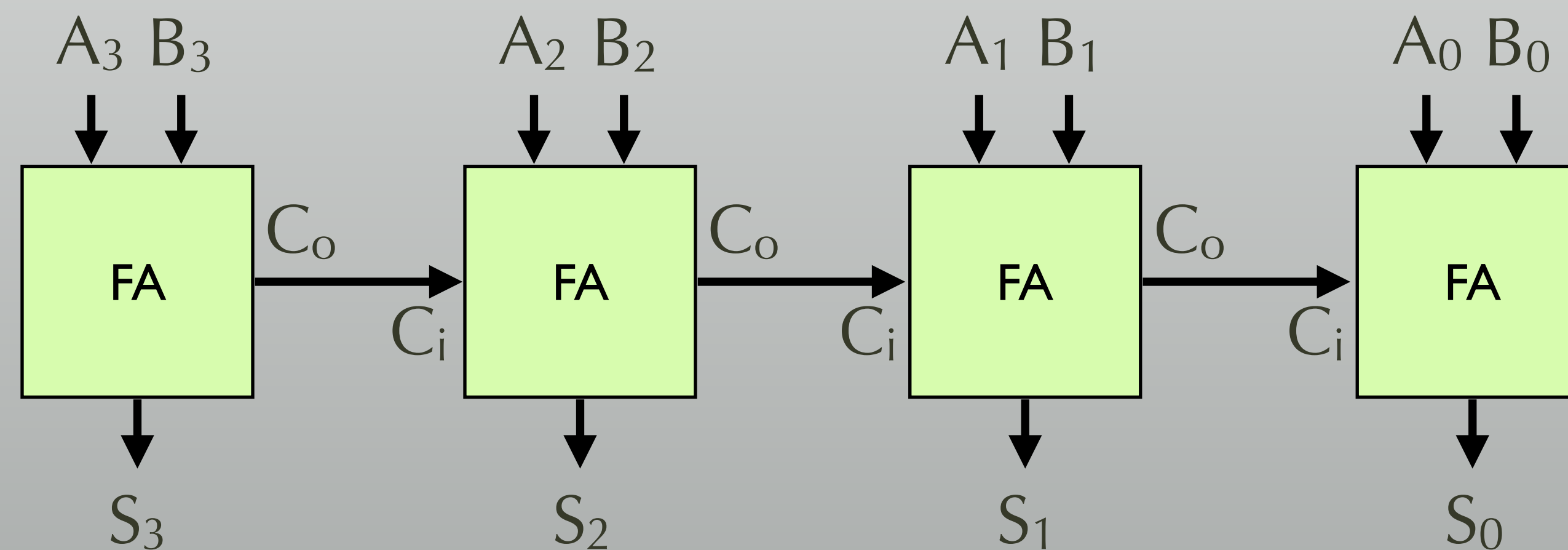
# Adders

- \* Daisy-chained full adders
  - \* A full adder can be implemented with an LUT
  - \* Problem is the carry chain delay



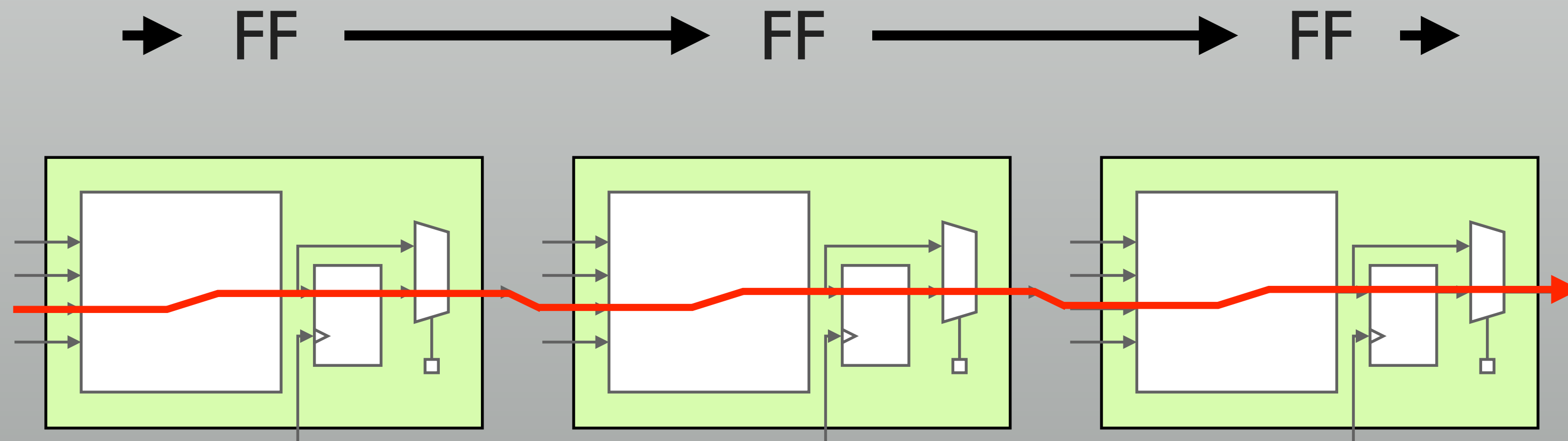
# Shift registers

- \* Daisy-chain of LBs
  - \* Delay is not problem, because there are (many) registers
  - \* LUTs are just “wires”: not very effective in resource usage


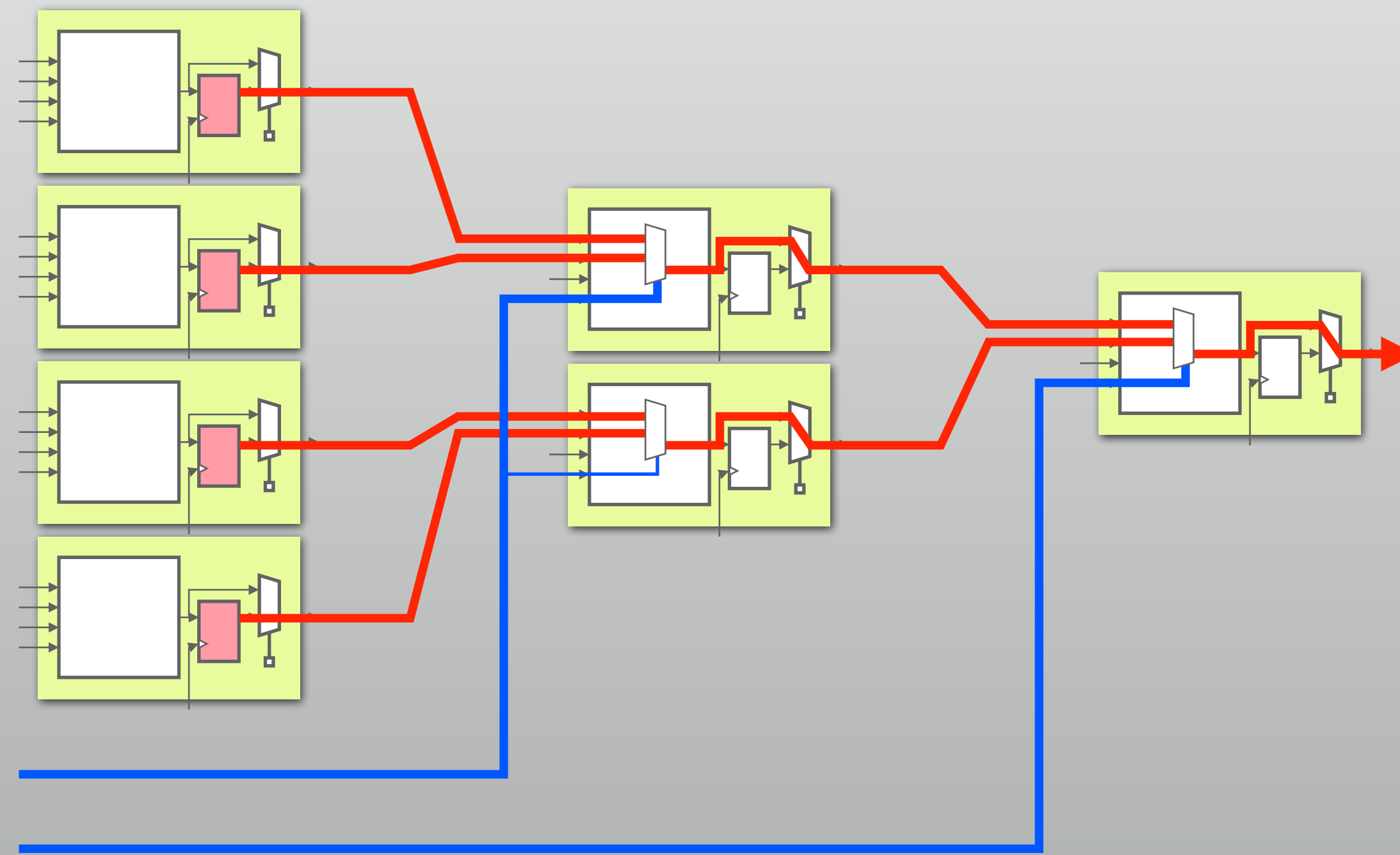
# Memory element

- \* LUTs are just to form address decoder...






# Ineffective?

- \* LUTs are SRAM cell
  - \* A 4-LUT has 16bits, a 6-LUT in modern FPGAs has 64bits
  - \* Of course, there's built-in address decoder
- \* LUTs are ready to be RAM cells, and maybe for shift registers and FIFOs


# Virtex-II LB organization

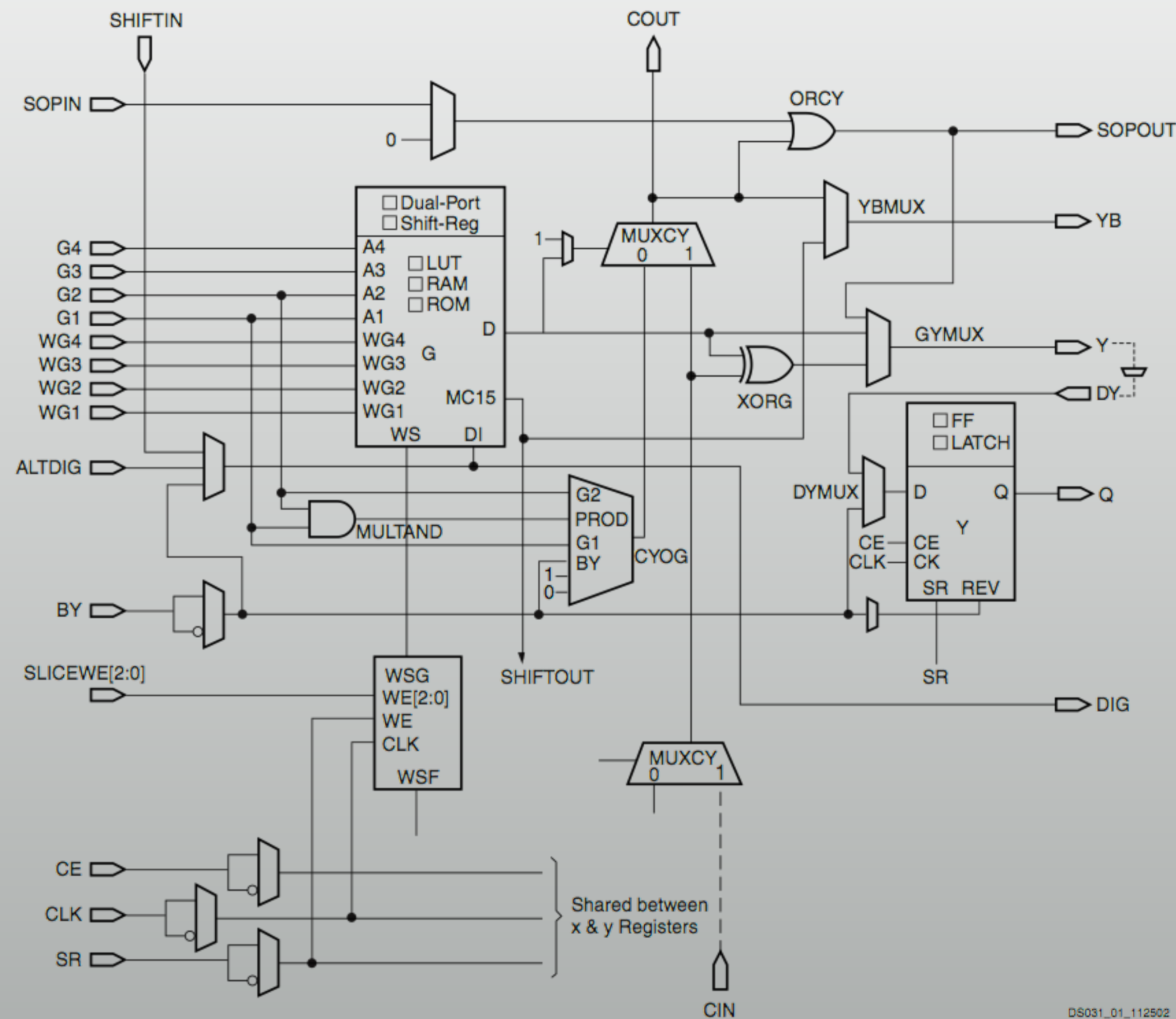

DS031\_01\_112502

Xilinx Virtex-II FPGA Datasheet (DS031) より


# As a basic LB...

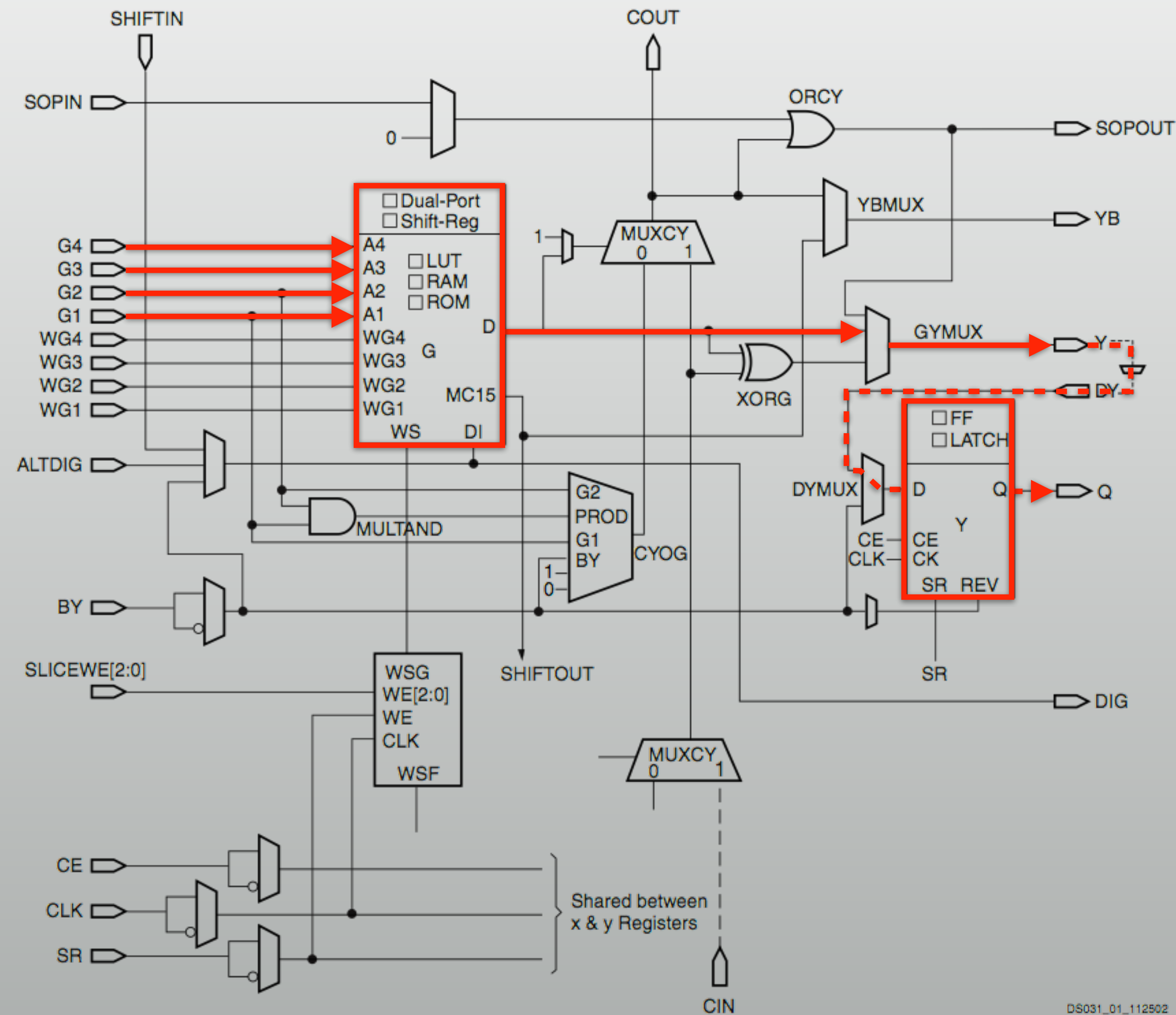

DS031\_01\_112502

Xilinx Virtex-II FPGA Datasheet (DS031) より


# As a dual-port memory cell

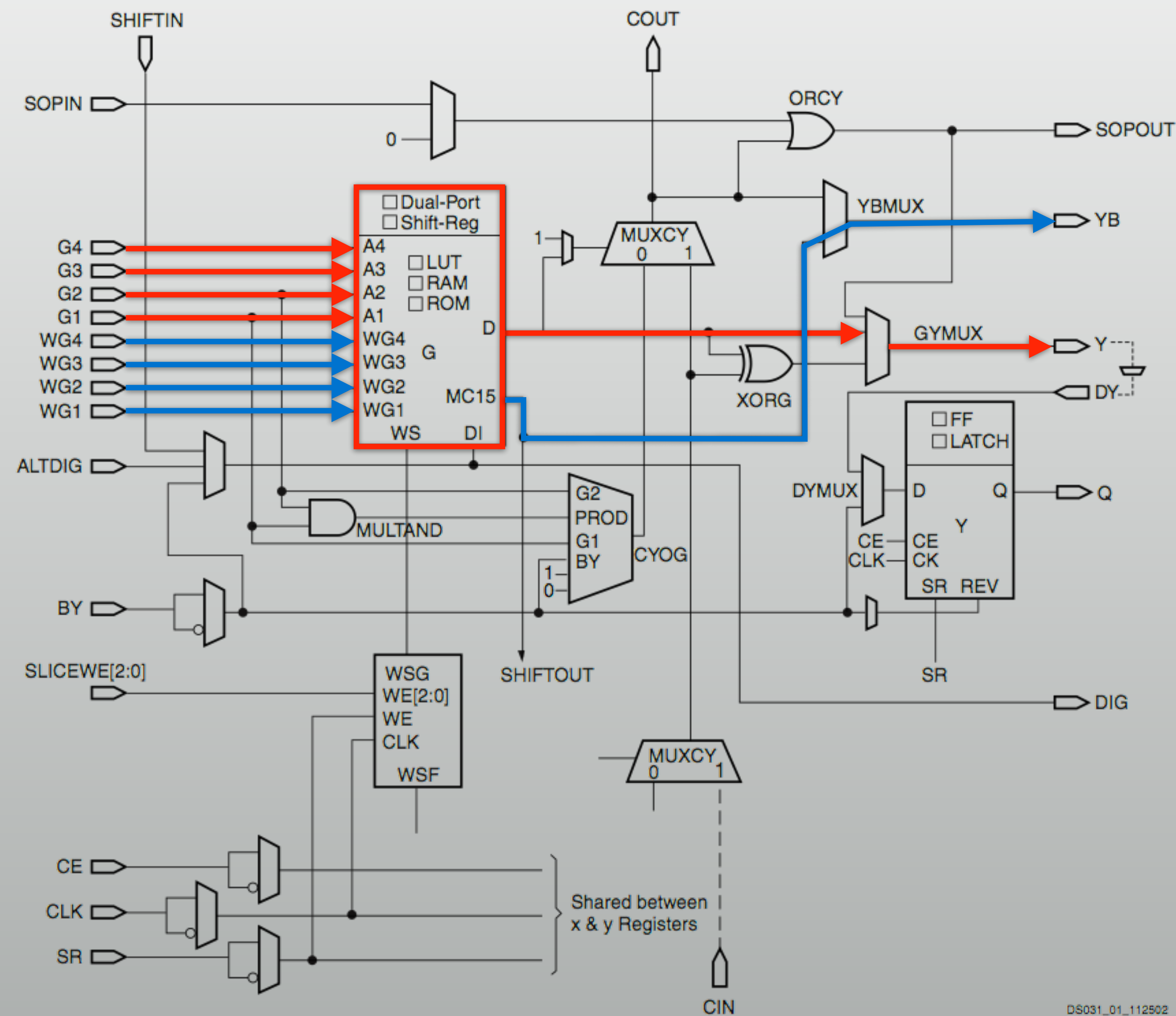

DS031\_01\_112502

Xilinx Virtex-II FPGA Datasheet (DS031) より


# Carry chain for adder

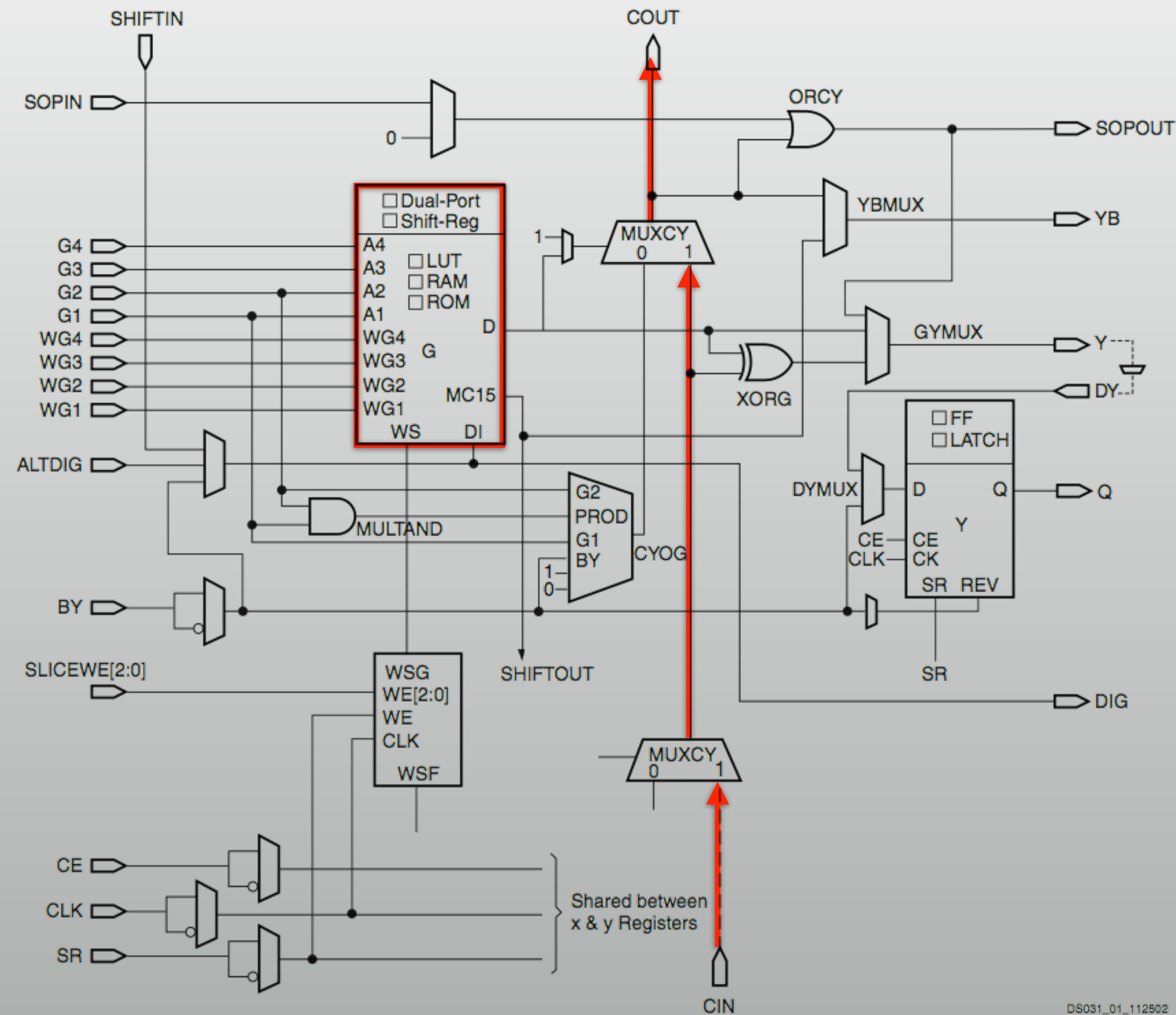

DS031\_01\_112502

Xilinx Virtex-II FPGA Datasheet (DS031) より

# Shift register chain

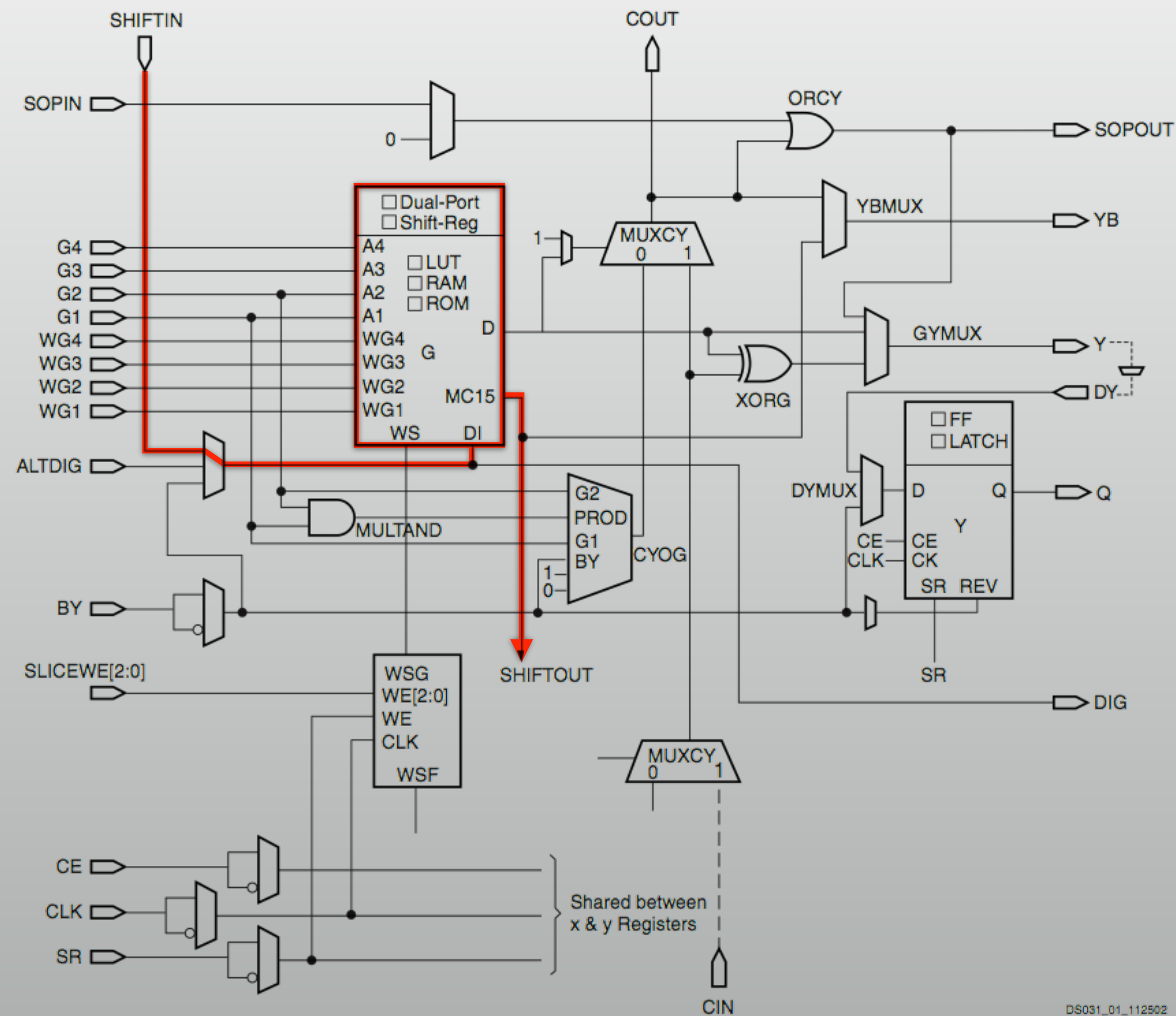

DS031\_01\_112502

Xilinx Virtex-II FPGA Datasheet (DS031) より



# LB+CB+SB=FPGA ?

- \* Indeed, it's not very effective
  - \* Go interconnection after every (LUT+FF+MUX) set
  - \* CB delay always follows to LB delay, is too slow
    - \* Sophisticated CLB (configurable logic block) provides shorter delay


# Flexibility and Performance

- \* CBs are not always necessary:
  - \* Making **clusters** of several LBs (LUT+FF+MUX sets)
  - \* Within the cluster, connections between LB without CB is possible
  - \* Of course, the LBs has connections with CBs, regardless of the cluster



 
# Clustering

- \* Local wires have simple organization
- \* Carry and shift register chains + some local logic wires


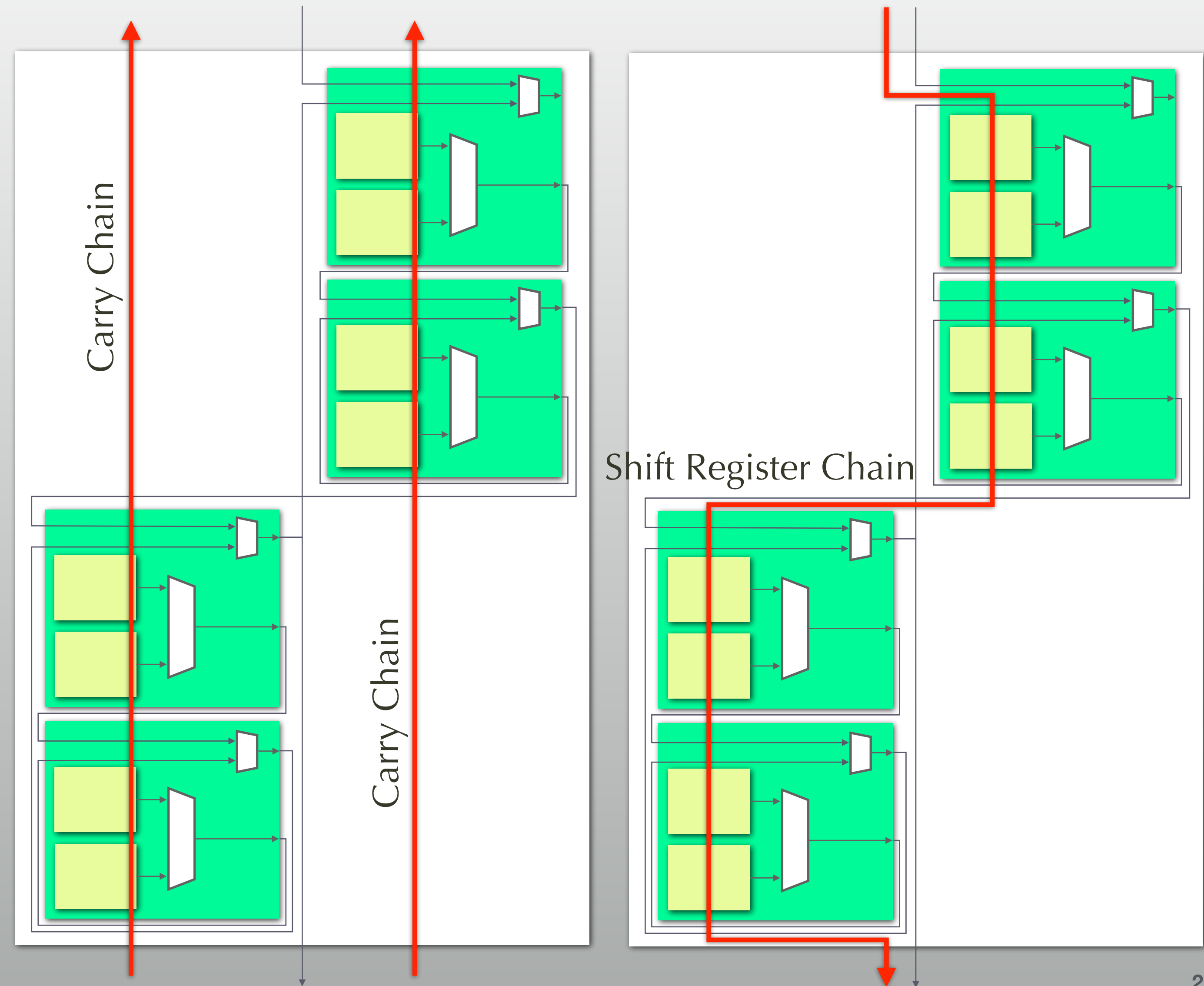
# Clustering

- \* Local wires have simple organization
- \* Carry and shift register chains + some local logic wires



# Interconnect architecture

- \* Very uniform structure, with wire segments of all same length is not good:
- \* Connecting more LBs in lower latency is important
- \* Use of some wire segments with different length helps
  - \* Same to the trains: local trains, rapid trains, express trains, ...


# Virtex-4 & 5

- \* Details are not officially disclosed
- \* Following slides are estimations from several documents from Xilinx
  - \* Not very accurate, but just for understanding of modern FPGA architecture

# Xilinx Virtex-4


- \* 3 wire types: Double (2 blocks), Hex (6 blocks) and Long (end-to-end)
- \* Double and Hex enables low-latency connections to neighbor LBs
- \* An extension to classical Xilinx FPGA architecture with double, quad and long

# Virtex-4 Interconnect

 


# Virtex-4 Interconnect

I Hop

 

# Virtex-4 Interconnect


2 Hops

 



# Virtex-4 Interconnect

3 Hops

 


# Xilinx Virtex-5

- \* Comes with 6-LUT
  - \* Simply, 50% more wires are required than 4-LUT
  - \* L-shaped wires (Pent) is introduced, instead of Hex wires
  - \* Enables connections with more neighbor LBs

# Virtex-5 Interconnect


I Hop

 

Single  
Double  
Pent


# Virtex-5 Interconnect

2 Hops

 

# Virtex-5 Interconnect

3 Hops

 


# Virtex-4 and Virtex-5

# Reachable CLBs

	Virtex-4	Virtex-5
1 Hop	12	12
2 Hops	68	96
3 Hops	200	180
Total	280	288

# Wire segments

	Virtex-4	Virtex-5
Double	40	42
Hex	120	-
Pent	-	120
Long	24	18
Total	184	180

 

# More wirings?

- \* Metal layers increases along the process technology, but no more...?
  - \* Virtex-II 150nm, 6 metal layers (2001)
  - \* Virtex-II Pro 130nm, 7 metal layers (2002)
  - \* Virtex-4 90nm, 10 metal layers (2004)
  - \* Virtex-5 65nm, 11 metal layers (2008)
  - \* Virtex-6 40nm, 12 metal layers (2009)
  - \* Virtex-7 28nm (2011)
  - \* Virtex Ultrascale 20nm (2014) / Ultrascale+ 16nm FinFET

# Input and output

- \* Classically:
  - \* TTL (5V), LVTTTL (3.3V)
  - \* CMOS (5V), LVCMOS (3.3V)
- \* Logic signals = board signals in these standards
  - \* With just drivers allowing more source/sink currents




# Classic, single-ended I/Os

- \* TTL/CMOS signals in 3.3 or 5V
  - \* High and Low in the voltage between GND
  - \* Simple circuits, but weak for noise and ground-bounces
  - \* Signal integrity problem with 66+MHz, such as reflections


# Faster single-ended I/Os

- \* Impedance matching and termination improves signal integrity

Damping resistors  
(series termination)

 

Thevenin termination

 


# Faster single-ended I/Os

- \* Use of active terminations
  - \* HSTL (High-speed transceiver logic) and SSTL (stub series terminated transceiver logic)
  - \* SSTL is commonly used in DDRx SDRAMs
  - \* With HSTL and SSTL, signal rate of 800~3000Mbps are possible
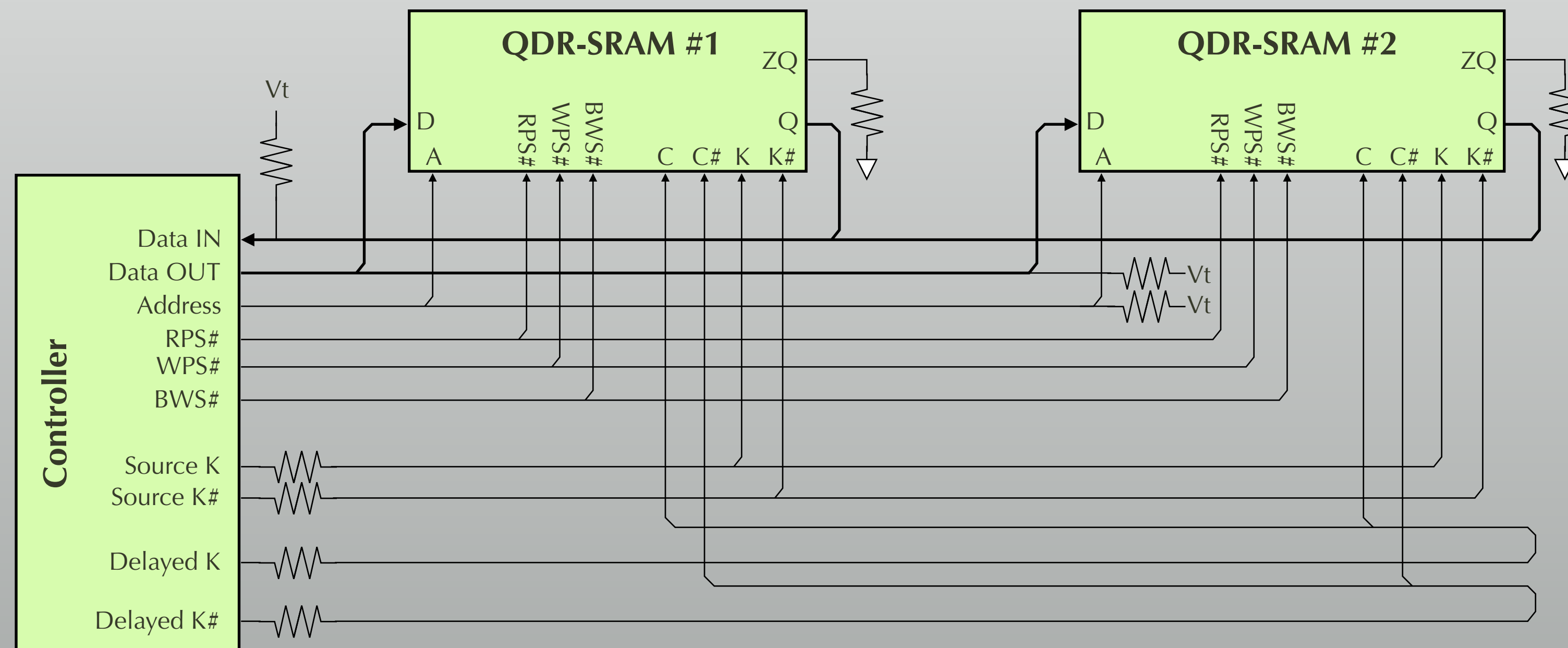
# HSTL

- \* Active terminations in all address + data signals, to reduce side effects of simultaneous switching
- \* Clock signals are with series terminations




$$V_t = V_{ddq}/2$$

# Differential signaling I/Os

- \* Much faster signal frequency with paired signal wires
  - \* LVDS, LVPECL, CML and more standards
- \* Popular in super-speed I/Os: PCI Express, USB, HDMI, ...
  - \* Several Gbps with 2 wires: 8~28Gbps per signal pair is available

 
# LVDS

- \* 3.5mA, current mode signaling (with 1.25V of common mode)
- \* With  $100\Omega$  termination: amplitude of 350mV



# Differential I/O standards

\* Power rails and amplitudes

 


# Many I/O standards are covered

- \* LVTTTL (3.3V)
- \* LVCMOS (3.3/2.5/1.5/1.2V)
- \* HSTL (1.8/1.5/1.2V)
- \* SSTL (2.5V/1.8V/1.5V)
- \* LVDS
- \* LVPECL
- \* GTL, GTL+
- \* (PCI, PCI-X)


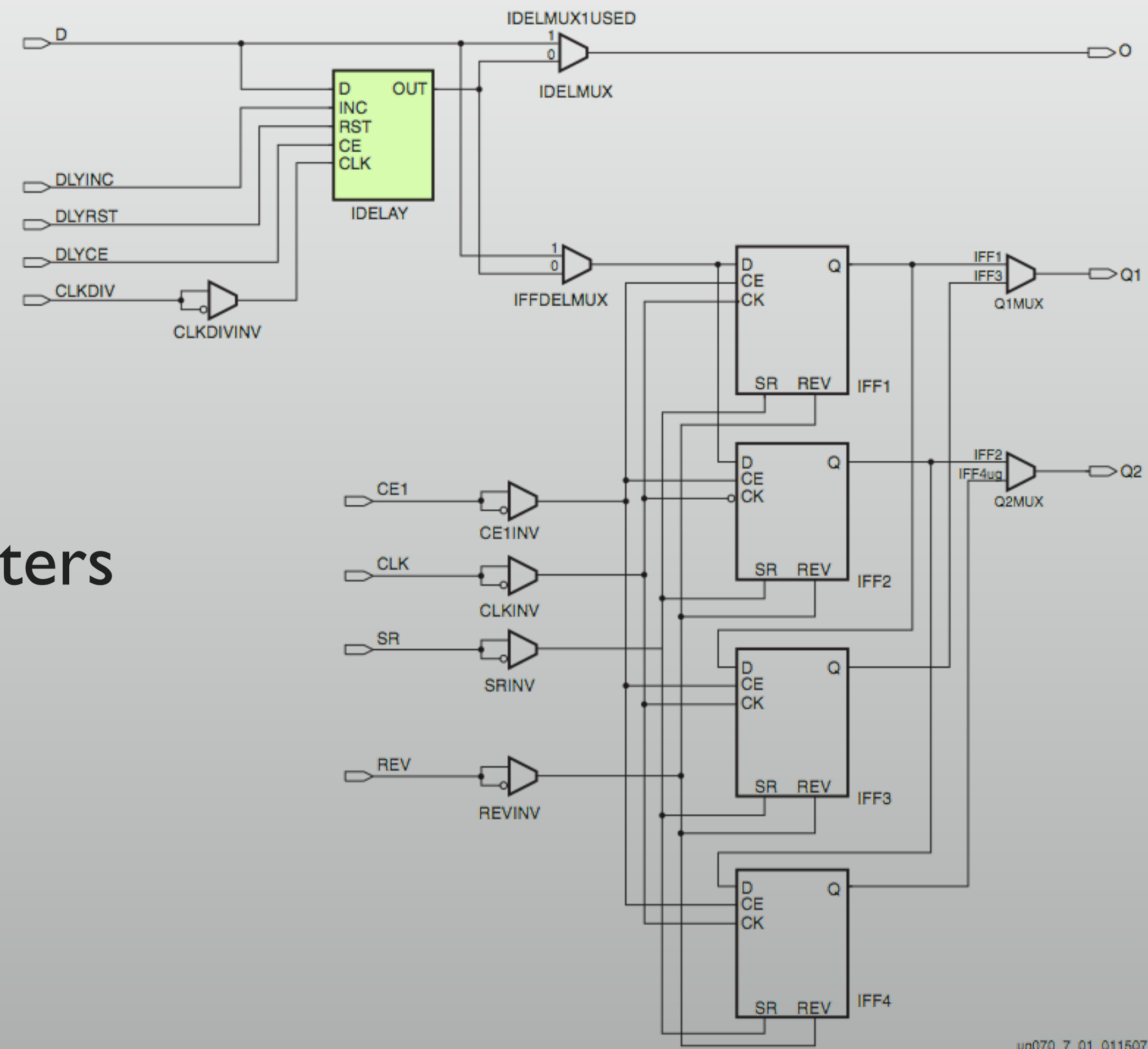
# On-chip I/O tweaks

- \* ILOGIC block in Virtex-4
- \* Not just an input buffer
- \* Delay element (IDELAY) and 4 registers
- \* Almost same for output



ug070\_7\_01\_011507

# Input registers

- \* Separating off-chip delays and on-chip delays
  - \* Off-chip delays are managed by the board designer
  - \* On-chip delays are managed by FPGA design tools such as Vivado
- \* These delays should be separated to make problems simple:
  - \* Placing registers on all I/O signals are highly recommended


# I/O registers

```
module some_fast_one
( input CLK, RST,
  input [7:0] A_IN,
  input      B_IN,
  . . . );

reg [7:0] A,
reg      B;

always @ (posedge CLK) begin
    A <= A_IN;
    B <= B_IN;
end

. . .
endmodule
```

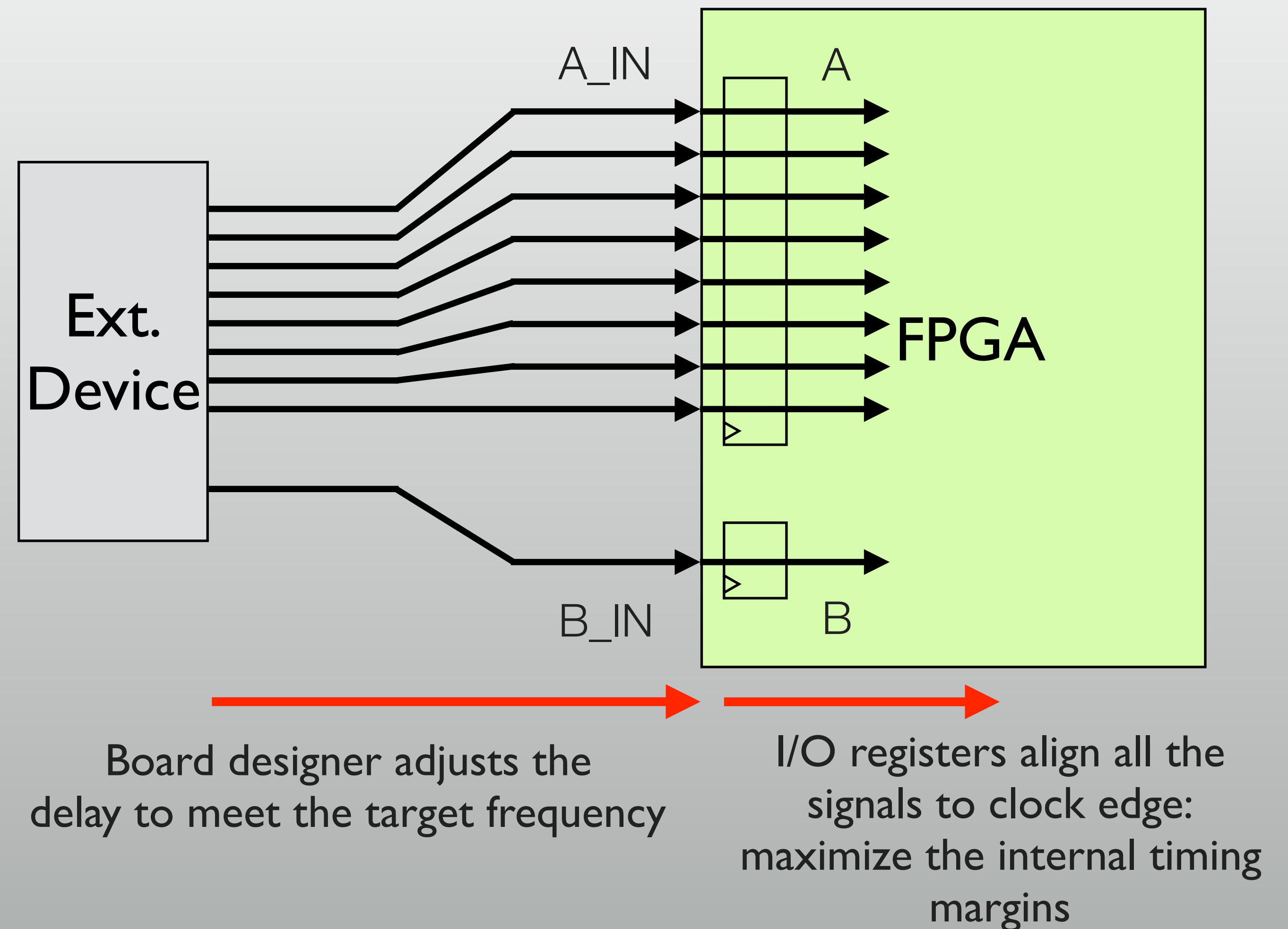

# DDR signals

- \* SDR (Single Data Rate):
  - \* Data signals are aligned on the positive edge of the clock signal
  - \* Data frequency =  $0.5 \times$  Clock frequency
- \* DDR (Double Data Rate):
  - \* Data signals are aligned on both clock edges: Data frequency = Clock freq.

# DDR signals in FPGA

- \* always @ (**CLK**) works in DDR
  - \* Works, but requires 1/2 of logic delay
  - \* Instead, internal SDR signals with 2x bit width is popular
    - \* DDR-2x SDR conversion is done by the I/O block registers
    - \* More timing margin in FPGA

# Example of input DDR

- \* 2 or 3 registers in IOB are used
- \* Some of them operates @ negedges


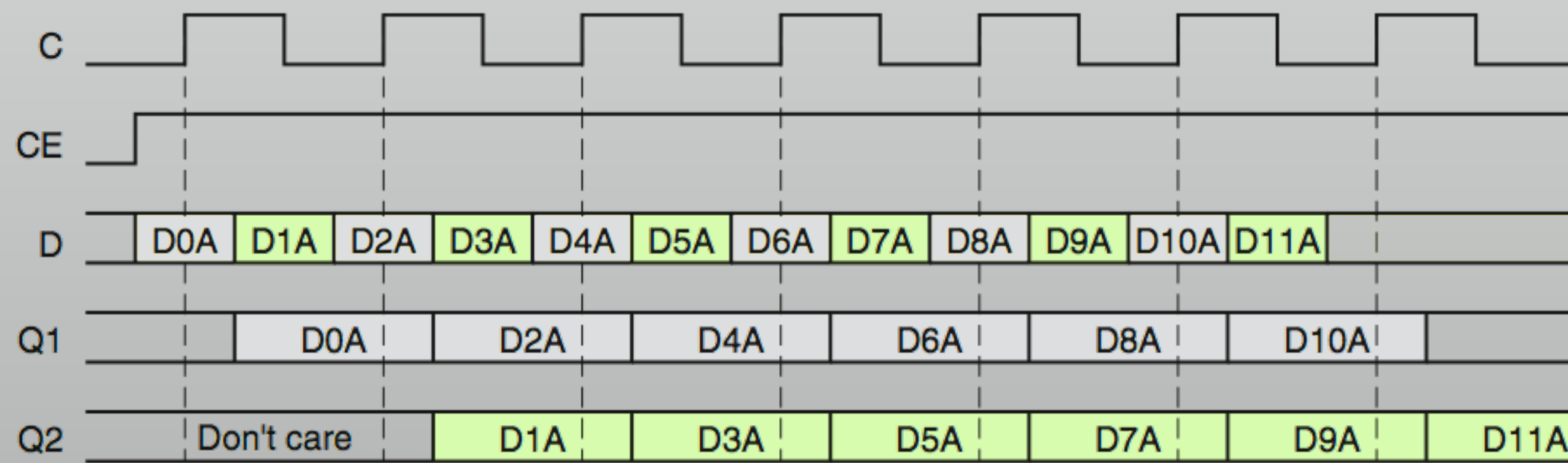


Figure 7-5: Input DDR Timing in SAME\_EDGE Mode

ug070\_7\_05\_072904

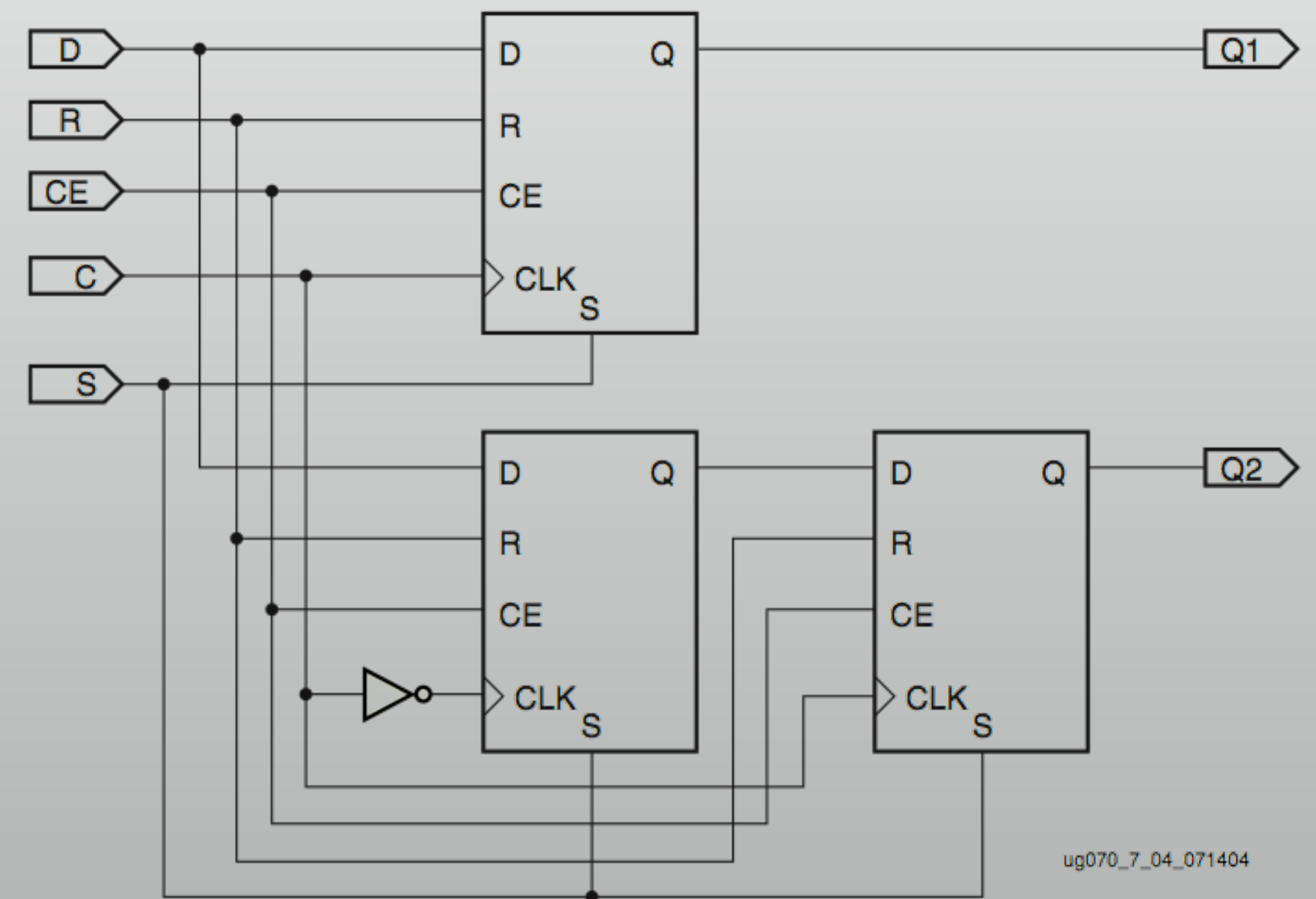

ug070\_7\_04\_071404


Figure 7-4: Input DDR in SAME\_EDGE Mode

# Delay element...?

- \* Shorter delay is better, but uniform delay is crucial
  - \* Wire delays are always slightly different in high-speed parallel bus
  - \* Fine-grain insertion of delay elements enables higher data rates or frequency
  - \* Independent delay elements on every input block: calibration with test pattern on system startup
 
# Clock tree

- \* A clock tree is driven by a clock buffer
- \* A clock buffer is driven by:
  - \* A clock capable pin, or special FPGA components such as CMT






# Clock Capable Pin

- \* Are very limited:
- \* Only half of them are available in single-ended
- \* Not all clock capable pins are same:  
detail follows

	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	
A	●	■	●	●	●	●	◐	●	●	●	○	■	●	●	●	●	◐	●	A
B	●	●	●	●	■	●	●	●	●	◐	○	●	●	●	■	●	●	●	B
C	○	○	◐	●	●	●	○	■	●	●	●	●	◐	●	●	◐	■	●	C
D	■	●	●	●	●	◐	⊗	○	⊗	⊗	■	○	⊗	●	●	◐	◐	●	D
E	○	●	●	■	●	●	○	⊕	C	K	I	M	O	■	●	●	◐	○	E
F	○	◐	●	●	s	⊗	■	■	■	■	■	■	●	●	●	●	■	◐	F
G	○	○	○	◐	○	■	■	■	■	■	■	■	s	B	◐	●	◐	●	G
H	○	○	■	○	○	■	■	■	■	■	■	■	○	⊗	●	◐	◐	■	H
J	◐	○	○	○	s	■	■	■	S	S	■	■	■	◐	◐	r	■	B	J
K	○	○	○	◐	○	s	■	■	S	S	■	■	■	◐	◐	r	s	B	K
L	○	■	○	○	⊗	○	■	■	L	J	■	■	B	○	B	◐	◐	○	L
M	○	○	○	○	■	○	■	■	■	■	■	■	⊗	○	■	○	○	○	M
N	○	○	◐	○	●	○	■	■	■	■	■	■	◐	○	●	●	○	■	N
P	■	○	●	●	●	◐	Y	■	P	D	2	0	1	○	●	◐	●	○	P
R	○	○	●	■	⊗	○	○	○	◐	s	s	○	○	■	●	U	●	○	R
T	○	◐	●	●	●	○	■	○	○	○	○	◐	○	●	●	B	■	○	T
U	○	○	○	○	◐	○	s	○	■	⊗	○	○	○	◐	○	○	○	○	U
V	○	○	■	○	○	○	○	◐	○	○	○	○	■	○	B	○	○	◐	V
	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	

 
# Global Clock

- \* Global Clock Buffer
  - \* Basically located at the center
  - \* Limited number



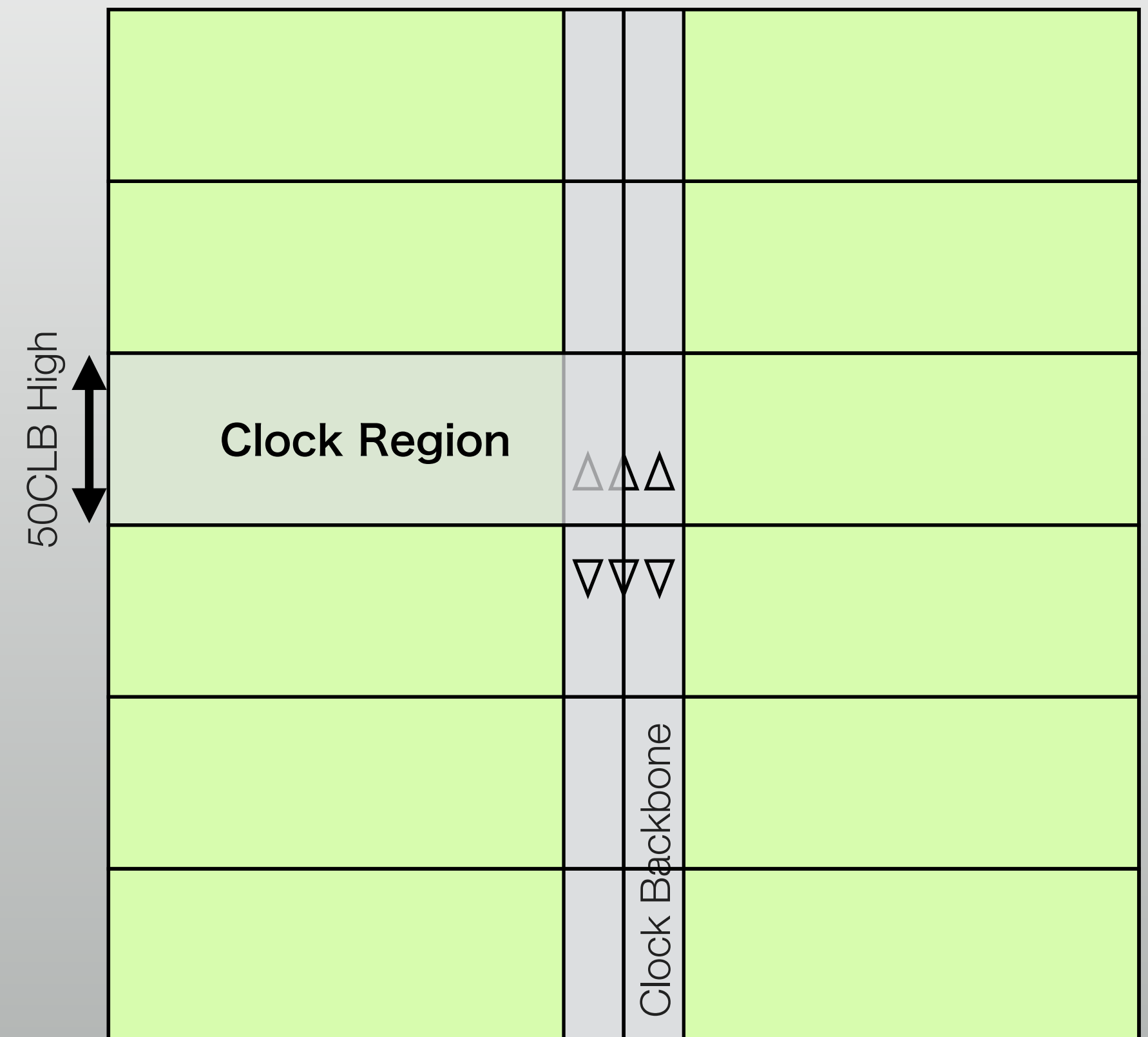
# Regional Clock

- \* Not all clock signals are required in everywhere
  - \* For example, memory controller requires several clock signals between memory devices and controller
- \* Regional clock is a good alternative
  - \* More # of clock signals are available


 
# Regional Clock

- \* Each clock region have:
  - \* Several clock capable I/O pins and
  - \* Several regional clock buffers
- \* In some devices, several clock region has their own clock management tiles



# Summary

- \* FPGA has basically uniform structure: LB, CB and SB
  - \* LB for programmable logic, CB+SB for programmable wires
  - \* Several dedicated components are essential: IO blocks and clock buffers
- \* More dedicated blocks are on modern FPGAs:
  - \* RAMs, DSPs, High-speed I/Os and CPUs: had no time to talk about this...

# Improves LB structure and functionality

- \* LUT + FF + MUX is the very basic
- \* Effectiveness for common building block is important
  - \* LUTs as memory elements or shift register
  - \* Carry chain for faster adder implementation

# Clustering: improves LB connectivity

- \* Adding direct LB connections in a cluster without requiring CB or SB
- \* Limited to simple structures, but powerful in:
  - \* Using 2 or more LUTs to form a larger LUT logic
  - \* Making longer shift-register chains or adder carry chains

# Improving interconnections

- \* Neighbor-to-neighbor connection is not perfect
  - \* Long-distance and multiple-destination connections are important
  - \* Availability of more # of destination LBs is crucial for better performance
    - \* Interconnection topology is a key of latest FPGA devices



# Off-chip I/Os

- \* Supports various single-ended and differential I/O standards
  - \* To connect with various external devices
- \* In several cases, on-FPGA termination registers are available to reduce on-board resistors
- \* Supports high-speed serial signals such as PCIe, USB or HDMI
  - \* Now FPGAs are used a hub of system

# On-chip I/Os

- \* I/O blocks have delay elements and registers
  - \* Delay elements enables the delay calibration on startup
  - \* Registers separates on- and off-chip delay, also useful for DDR operations

# Clock resources

- \* Dedicated clock input pins, clock buffers and clock-tree wires
  - \* Global clocks reaches to everywhere on FPGA
    - \* Global clock signals are synthesized in RTL without special cares
    - \* Explicit use of regional clock enables to use local clock signals for several modules, such as external memory controllers