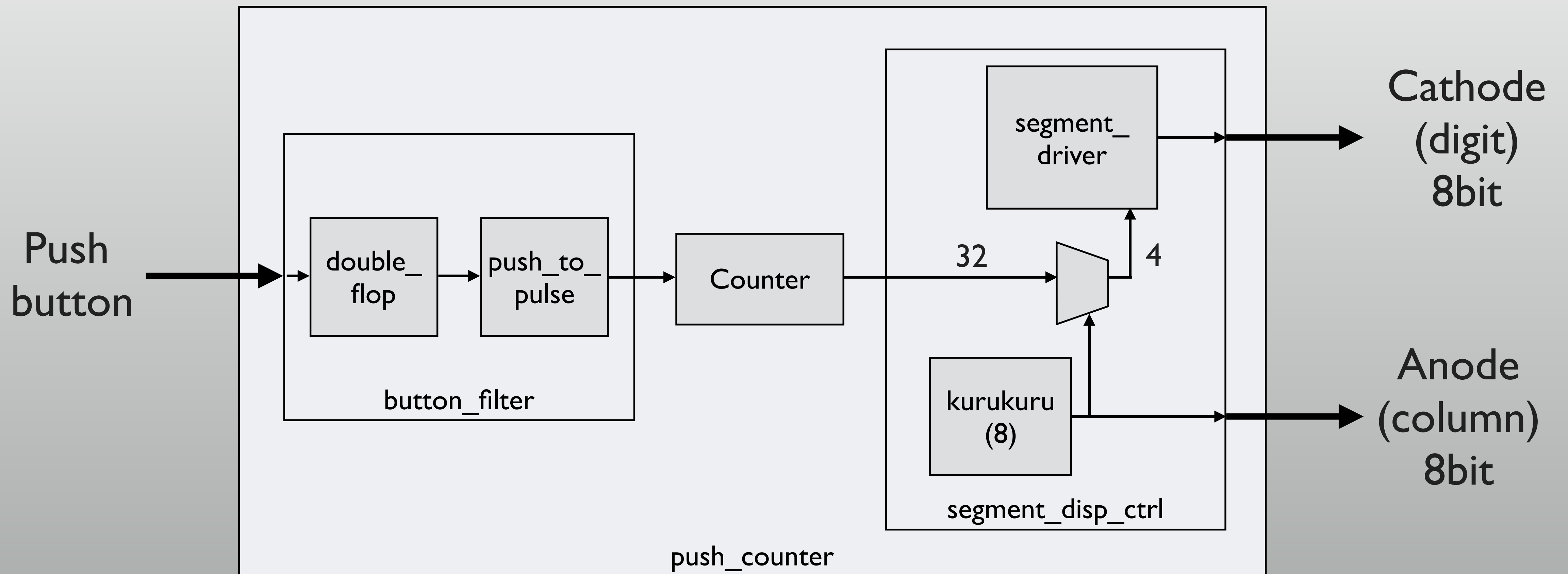



Reconfigurable Architecture (13)

Code Review

Making a stopwatch: the base design



Basic organization

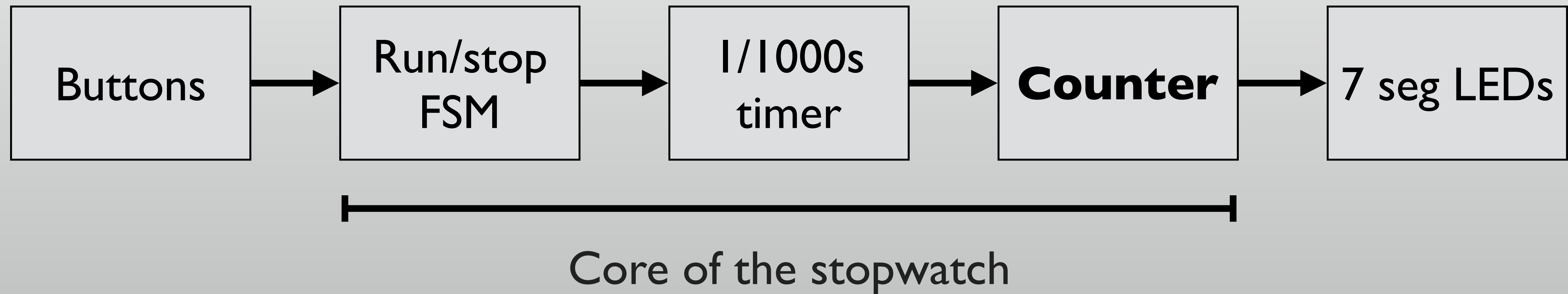


2 Strategies

Original: binary counter



Strategy 1:
Binary counter + Bin-Dec converter

 

Strategy 2:
Making a decimal counter



Binary (Hexadecimal) to Decimal

- * Requires dividers by 10
- * Quotient and remainder
- * Results in very slow or very large circuit

```
1  begin
2      case (LED_activating_counter)
3          2'b00: begin
4              Anode_Activate = 4'b0111;
5              LED_BCD = displayed_number/1000;
6          end
7          2'b01: begin
8              Anode_Activate = 4'b1011;
9              LED_BCD = (displayed_number % 1000)/100;
10         end
11         2'b10: begin
12             Anode_Activate = 4'b1101;
13             LED_BCD = ((displayed_number % 1000)%100)/10;
14         end
15         2'b11: begin
16             Anode_Activate = 4'b1110;
17             LED_BCD = ((displayed_number % 1000)%100)%10;
18         end
19     endcase
20 end
```

Implementation Result for 4 digits

- * Working at 100MHz is possible
- * Delay \approx 8ns
- * Requires 13% of BlockRAM!
(for only bin-dec conversion)

Timing

Worst Negative Slack (WNS):	2.043 ns
Total Negative Slack (TNS):	0 ns
Number of Failing Endpoints:	0
Total Number of Endpoints:	7258

[Implemented Timing Report](#)

Resource	Utilization	Available	Utilization %
LUT	2411	63400	3.80
LUTRAM	199	19000	1.05
FF	2223	126800	1.75
BRAM	18	135	13.33
IO	4	210	1.90
BUFG	2	32	6.25

Making a decimal counter

- * else if else if else if else if...
- * Maintenance is hard

```
1  reg [ 3:0] cnt1;
2  reg [ 3:0] cnt2;
3  reg [ 3:0] cnt3;
4  reg [ 3:0] cnt4;
5  always @ (posedge CLK) begin
6      if (RST) begin
7          cnt1 <= 0;
8          cnt2 <= 0;
9          cnt3 <= 0;
10         cnt4 <= 0;
11     end else if (PLUS) begin
12         if (cnt4 == 10) begin
13             cnt1 <= 0;
14             cnt2 <= 0;
15             cnt3 <= 0;
16         end else if (cnt3 == 10) begin
17             cnt4 <= cnt4 + 1;
18             cnt3 <= 0;
19         end else if (cnt2 == 10) begin
20             cnt3 <= cnt3 + 1;
21             cnt2 <= 0;
22         end else if (cnt1 == 10) begin
23             cnt2 <= cnt2 + 1;
24             cnt1 <= 0;
25         end else begin
26             cnt1 <= cnt1 + 1;
27         end
28     end
29 end
```

Oh, no...

- * With a single register, but still not good for maintenance

```
1  reg [15:0]  COUNTER;
2  always @ (posedge CLK) begin
3      if (RST) begin
4          COUNTER <= 0;
5      end
6      else begin
7          if (PLUS) begin
8              COUNTER<=COUNTER+1;
9          end
10         else if (COUNTER[3:0]==10) begin
11             COUNTER[7:4] <=COUNTER[7:4]+1;
12             COUNTER[3:0] <=0;
13         end
14         else if (COUNTER[7:4]==10) begin
15             COUNTER[11:8] <=COUNTER[11:8]+1;
16             COUNTER[7:0] <=0;
17         end
18         else if (COUNTER[11:8]==10) begin
19             COUNTER[15:12] <=COUNTER[15:12]+1;
20             COUNTER[11:0] <=0;
21         end
22         else if (COUNTER[15:12]==10) begin
23             COUNTER[19:16] <=COUNTER[19:16]+1;
24             COUNTER[15:12] <=0;
25         end
26     end
27 end
```


A little bit more uniform way

- * Separate description for each column
- * “Never write same thing more than once” rule in programming

```
1 // 0.001
2 always @( posedge CLK ) begin
3     if( CLR )
4         QA <= 4'd0;
5     else if( EN==1'b1 ) begin
6         if( QA==4'd9 )
7             QA <= 4'd0;
8         else
9             QA <= QA + 1'b1;
10    end
11 end
12
13 // 0.001
14 always @( posedge CLK ) begin
15     if( CLR )
16         QB <= 4'd0;
17     else if( EN==1'b1 && QA==4'd9 ) begin
18         if( QB==4'd9 )
19             QB <= 4'd0;
20         else
21             QB <= QB + 1'b1;
22    end
23 end
```

Using modularity

- * Encapsulate the counter in dec_cnt
- * Reuse for every columns
- * Can be extended to any # of columns easily

```
1 module dec_cnt
2   ( input wire CLK, RST,
3     input wire    CIN,
4     output wire   COUT,
5     output reg [3:0] VAL);
6
7   always @ (posedge CLK) begin
8     if (RST) begin
9       VAL <= 0;
10    end else begin
11      if (CIN) begin
12        VAL <= (VAL==9) ? 0 : VAL+1;
13      end
14    end
15  end
16
17  assign COUT = (VAL==9) & CIN;
18 endmodule
19
20 module dec_cnt4
21   ( input wire CLK, RST,
22     input wire    TIME,
23     output wire [15:0] VAL);
24
25   wire [3:0]    C;
26
27   dec_cnt c1 (.CLK(CLK), .RST(RST), .CIN(TIME), .COUT(C[0]), .VAL(VAL[ 3: 0]));
28   dec_cnt c2 (.CLK(CLK), .RST(RST), .CIN(C[0]), .COUT(C[1]), .VAL(VAL[ 7: 4]));
29   dec_cnt c3 (.CLK(CLK), .RST(RST), .CIN(C[1]), .COUT(C[2]), .VAL(VAL[11: 8]));
30   dec_cnt c4 (.CLK(CLK), .RST(RST), .CIN(C[2]), .COUT(C[3]), .VAL(VAL[15:12]));
31 endmodule
```

Implementation Results

- * Very small and fast
- * delay < 4ns
- * 1/200 LUT, 1/100 FF compared to bin-dec converter

Timing	Setup
Worst Negative Slack (WNS):	6.185 ns
Total Negative Slack (TNS):	0 ns
Number of Failing Endpoints:	0
Total Number of Endpoints:	28

Resource	Utilization	Available	Utilization %
LUT	11	63400	0.02
FF	16	126800	0.01
IO	19	210	9.05
BUFG	1	32	3.13

Basic design principle: three-Y's

- * Hierarchy: dividing a system into modules, further sub-dividing of modules until the pieces are easy to understand
- * Modularity: modules have well-defined functions and interfaces, can be connected together easily without unanticipated side-effects
- * Regularity: seek uniformity among the modules, common modules are reused